

CSC 252: Computer Organization

Spring 2019: Lecture 12

Instructor: Yuhao Zhu

Department of Computer Science
University of Rochester

Action Items:

- **Assignment 3 is due March 1, midnight**

Announcement

- Programming Assignment 3 is due on **March 1, midnight**
- Mid-term exam: **March 7**; in class
- Past exam & Problem set: <http://www.cs.rochester.edu/courses/252/spring2019/handouts.html>

MON 25	TUE 26	WED 27	THU 28	FRI Mar 1
	Lecture		Lecture	A3 due
4	5	6	7	8
	Lecture		Midterm	

The Need for Storing Bits

- Assembly programs set architecture (processor) states.
 - Register File
 - Status Flags
 - Memory
 - Program Counter

The Need for Storing Bits

- Assembly programs set architecture (processor) states.
 - Register File
 - Status Flags
 - Memory
 - Program Counter
- Every state is essentially some bits that are stored/loaded.

The Need for Storing Bits

- Assembly programs set architecture (processor) states.
 - Register File
 - Status Flags
 - Memory
 - Program Counter
- Every state is essentially some bits that are stored/loaded.
- Think of the program execution as an FSM.


The Need for Storing Bits

- Assembly programs set architecture (processor) states.
 - Register File
 - Status Flags
 - Memory
 - Program Counter
- Every state is essentially some bits that are stored/loaded.
- Think of the program execution as an FSM.
- The hardware must provide mechanisms to load and store bits.

The Need for Storing Bits

- Assembly programs set architecture (processor) states.
 - Register File
 - Status Flags
 - Memory
 - Program Counter
- Every state is essentially some bits that are stored/loaded.
- Think of the program execution as an FSM.
- The hardware must provide mechanisms to load and store bits.
- There are many different ways to store bits. They have trade-offs.


Build a 1-Bit Storage

 

- What I would like:
 - D is the data I want to store (0 or 1)
 - C is the control signal
 - When C is 1, Q becomes D (i.e., storing the data)
 - When C is 0, Q doesn't change with D (data stored)

Building Block: RS Latch


Bistable Element

 


$q = 0 \text{ or } 1$

Building Block: RS Latch

Bistable Element

 


$q = 0$ or 1


 


Building Block: RS Latch

Bistable Element

 


$q = 0$ or 1


 
 


Building Block: RS Latch

Bistable Element

 


$q = 0$ or 1


 
 
 


Building Block: RS Latch

Bistable Element

 


$q = 0$ or 1

    





Building Block: RS Latch

Bistable Element

 


$q = 0$ or 1


R-S Latch

    


A Simple Way of Storing/Accessing 1 Bit

 


A Simple Way of Storing/Accessing 1 Bit

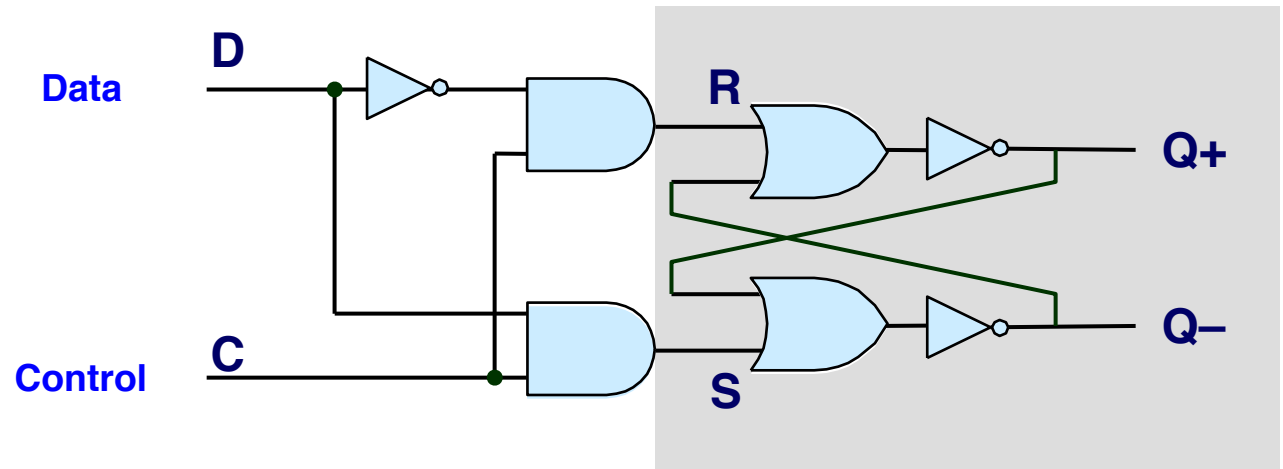


Storing 1

 


A Simple Way of Storing/Accessing 1 Bit

 


Storing 1

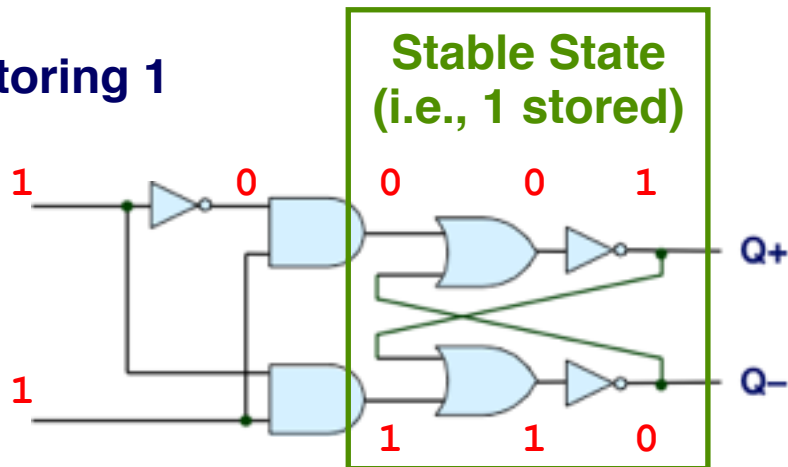

A Simple Way of Storing/Accessing 1 Bit

 


Storing 1

 


When C is 1, D is 1, Q+ will eventually become 1.

A Simple Way of Storing/Accessing 1 Bit

 


Storing 1



 


When C is 1, D is 1, Q+ will eventually become 1.

Storing 0

 


A Simple Way of Storing/Accessing 1 Bit

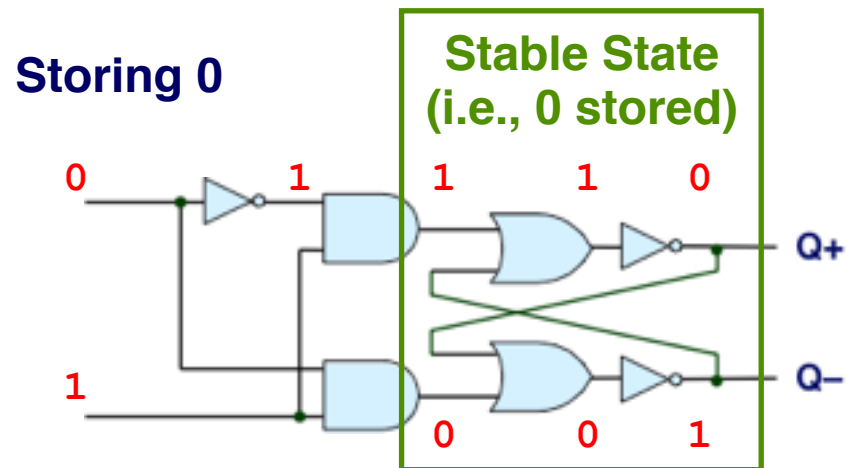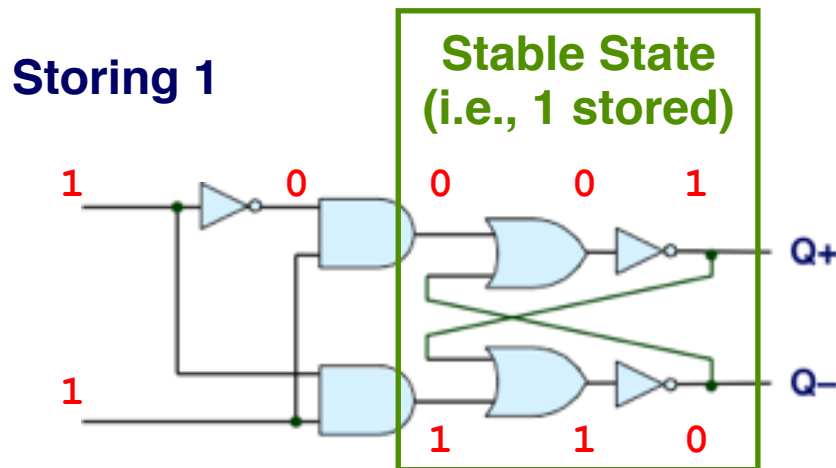 


When C is 1, D is 1, Q+ will eventually become 1.

A Simple Way of Storing/Accessing 1 Bit

 


Storing 1

 

When C is 1, D is 1, Q+ will eventually become 1.


Storing 0

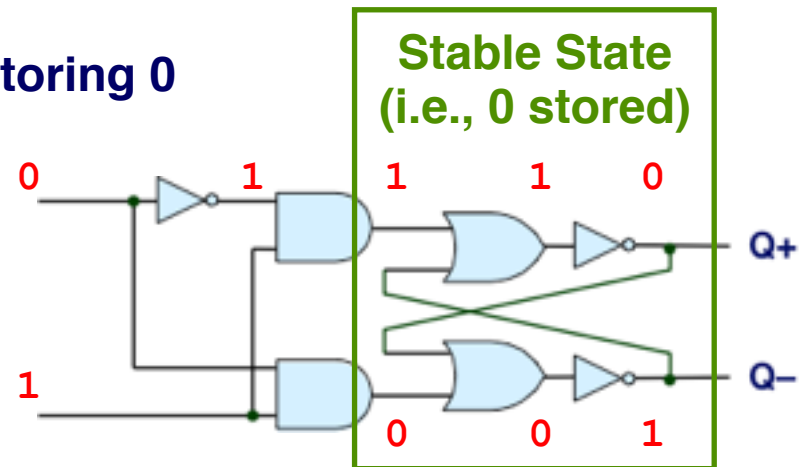


When C is 1, D is 0, Q+ will eventually become 0.

A Simple Way of Storing/Accessing 1 Bit

D Latch

 


Storing 1

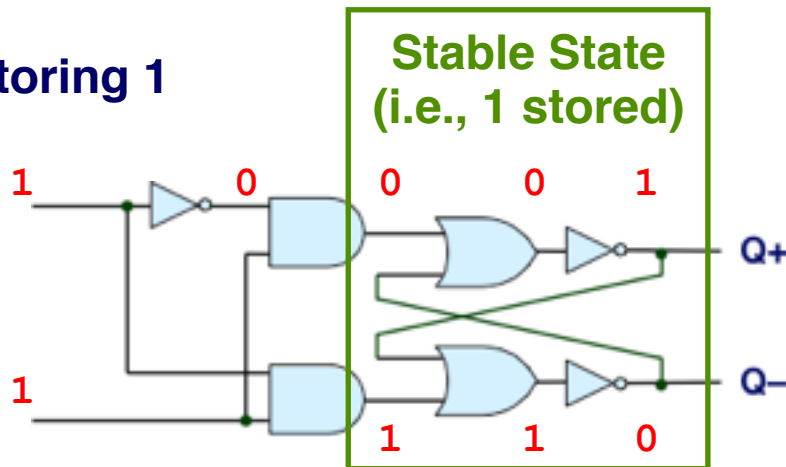

When C is 1, D is 1, Q+ will eventually become 1.


Storing 0

 


When C is 1, D is 0, Q+ will eventually become 0.

A Simple Way of Storing/Accessing 1 Bit

D Latch

 


Holding Data

 


A Simple Way of Storing/Accessing 1 Bit

D Latch

 


Holding Data

 


If $C == 0$, $Q+$ doesn't change with d

A Simple Way of Storing/Accessing 1 Bit

D Latch

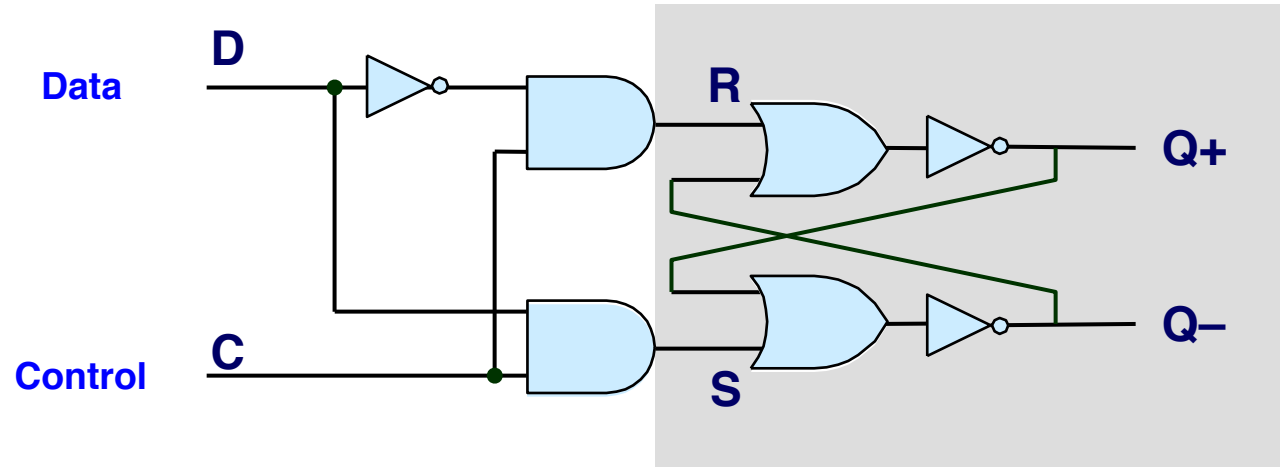


Holding Data

 


If C == 0, Q+ doesn't change with d

D-Latch is “Transparent”

Latching

 


Changing D

 


D-Latch is “Transparent”

Latching

 


Changing D

 


D-Latch is “Transparent”

Latching

 


Changing D

 


D-Latch is “Transparent”

Latching

 


Changing D

 


D-Latch is “Transparent”

Latching

 


Changing D

 


D-Latch is “Transparent”

Latching

 


Changing D

 


D-Latch is “Transparent”

Latching

 


Changing D

 


D-Latch is “Transparent”

Latching

 


Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**

D-Latch is “Transparent”

Latching

 


Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+** and **Q-**. So hold C for a while until the signal is fully propagated

D-Latch is “Transparent”

Latching

 


Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+** and **Q-**. So hold C for a while until the signal is fully propagated
- Then set **C** to 0. Value latched depends on value of **D** as **C** goes to 0

D-Latch is “Transparent”

Latching

 


Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+** and **Q-**. So hold C for a while until the signal is fully propagated
- Then set **C** to 0. Value latched depends on value of **D** as **C** goes to 0
- D-latch is *transparent* when **C** is 1

D-Latch is “Transparent”

Latching

 


Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+** and **Q-**. So hold C for a while until the signal is fully propagated
- Then set **C** to 0. Value latched depends on value of **D** as **C** goes to 0
- D-latch is *transparent* when **C** is 1
- D-latch is “*level-triggered*” b/c **Q** changes as the voltage level of **C** rises.


Edge-Triggered Latch (Flip-Flop)

 


Edge-Triggered Latch (Flip-Flop)

 


Edge-Triggered Latch (Flip-Flop)

 


Edge-Triggered Latch (Flip-Flop)

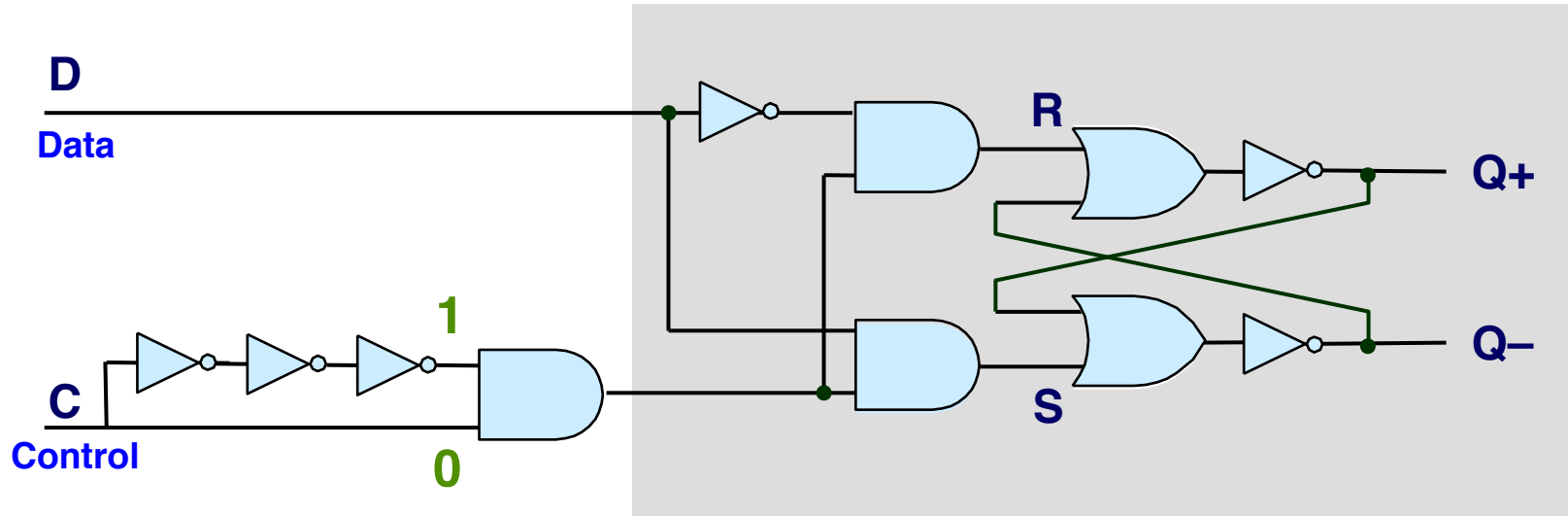


Edge-Triggered Latch (Flip-Flop)

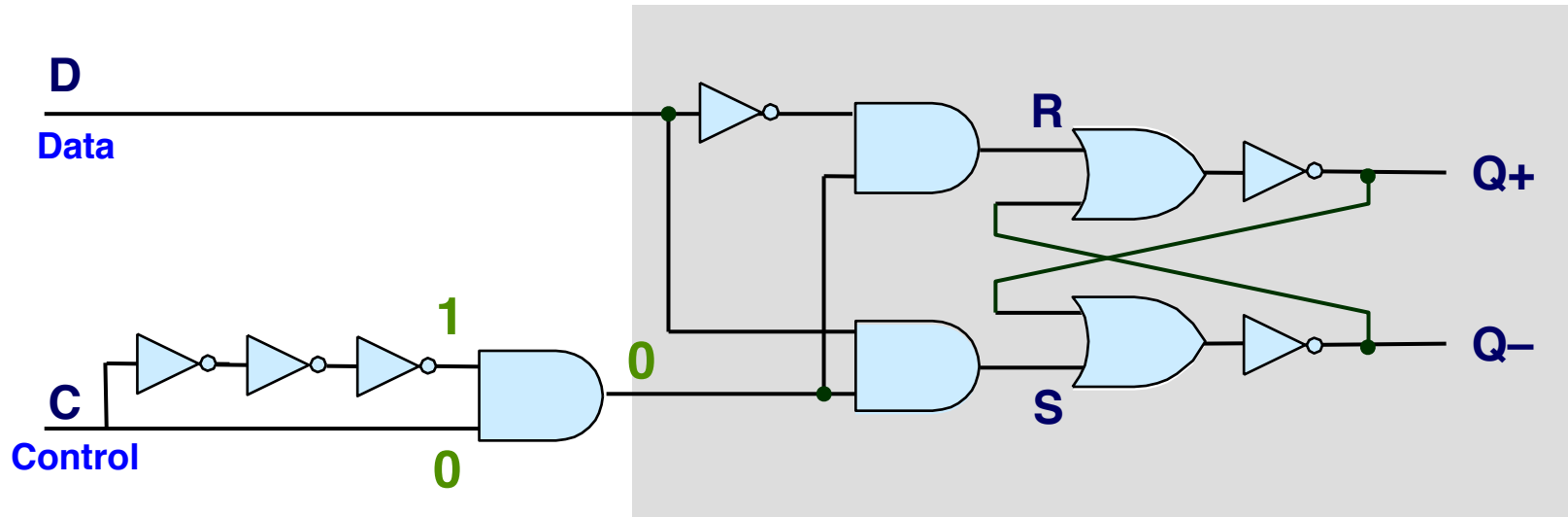


Edge-Triggered Latch (Flip-Flop)

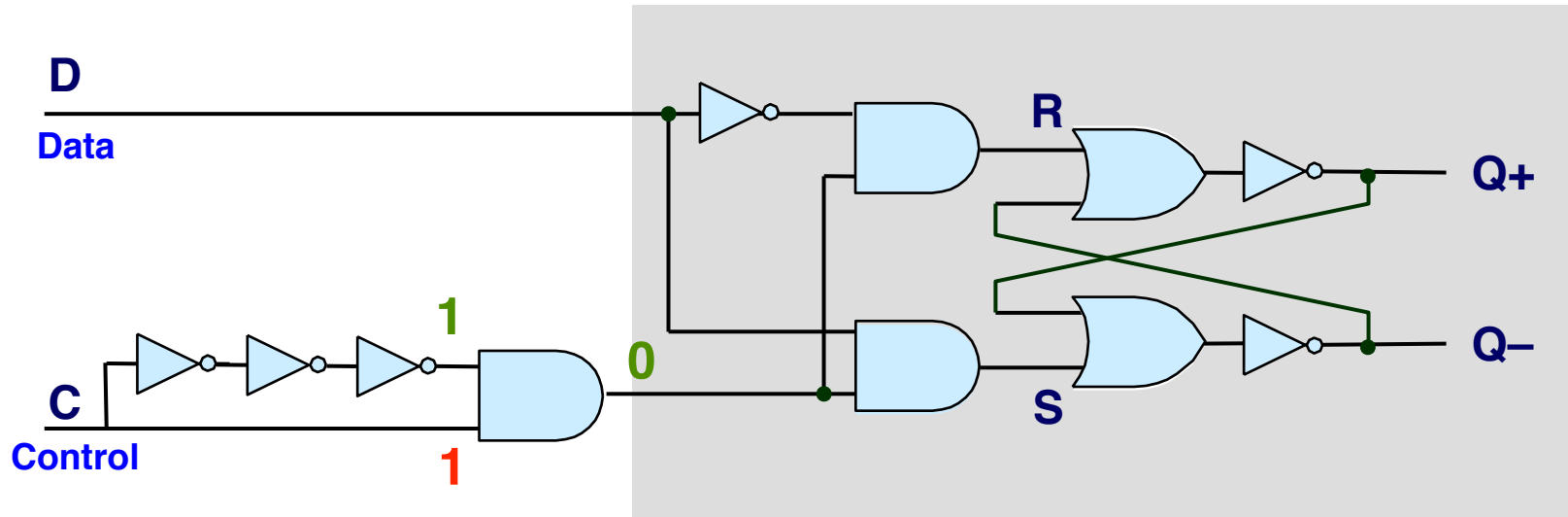


Edge-Triggered Latch (Flip-Flop)

 



Edge-Triggered Latch (Flip-Flop)

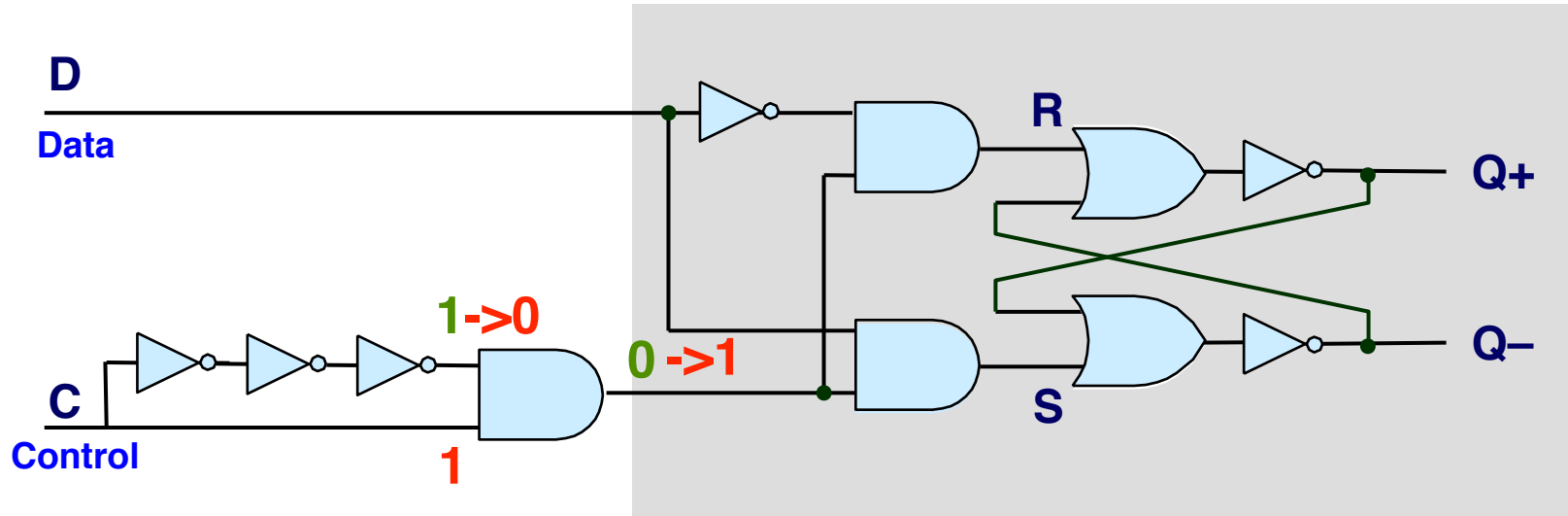



Edge-Triggered Latch (Flip-Flop)

 

Edge-Triggered Latch (Flip-Flop)

 
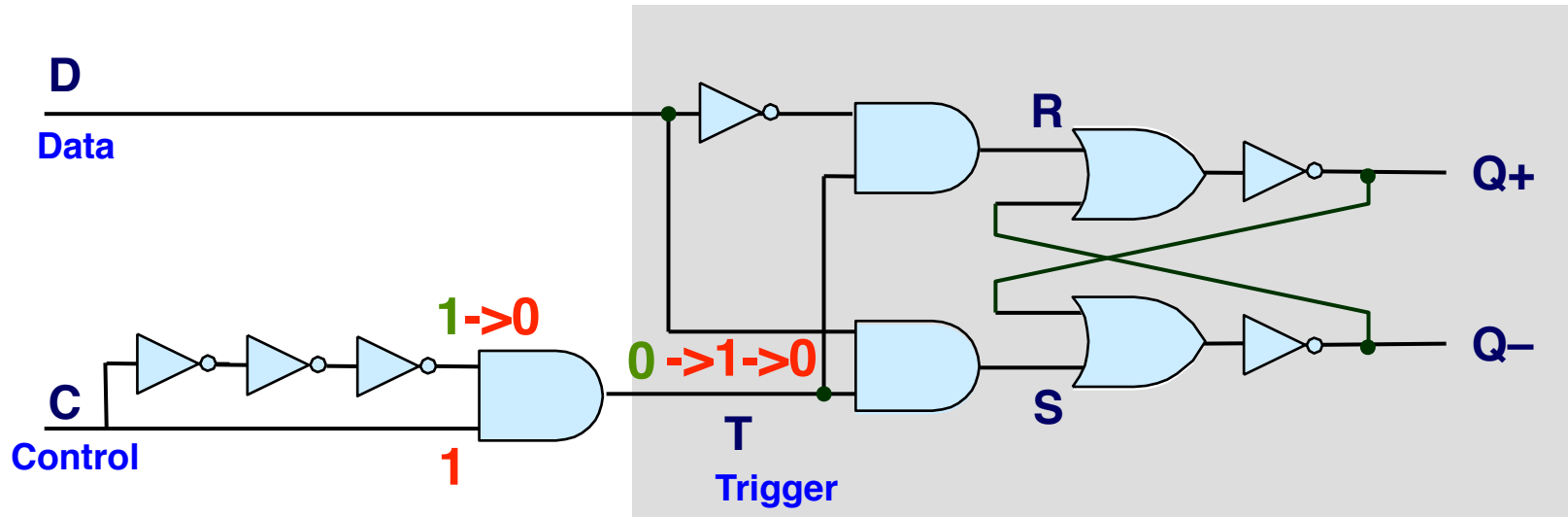


Edge-Triggered Latch (Flip-Flop)

  



- Flip-flop: Only latches data for a brief period

Edge-Triggered Latch (Flip-Flop)

  


- Flip-flop: Only latches data for a brief period
- Value latched depends on data as **C rises** (i.e., $0 \rightarrow 1$); usually called at the **rising edge** of **C**

Edge-Triggered Latch (Flip-Flop)

  



- Flip-flop: Only latches data for a brief period
- Value latched depends on data as C **rises** (i.e., 0→1); usually called at the **rising edge** of C
- Output remains stable at all other times

Registers

 


- Stores several bits of data
- Collection of edge-triggered latches (D Flip-flops)
- Loads input on rising edge of the C signal

Registers

  


- Stores several bits of data
- Collection of edge-triggered latches (D Flip-flops)
- Loads input on rising edge of the C signal


Register Operation

 


Register Operation

 

Register Operation

 


Register Operation

 

- Stores data bits
- For most of time acts as barrier between input and output
- As C rises, loads input
- So you'd better compute the input before the C signal rises if you want to store the input data to the register


Register Operation

 

Output **continuously** produces y after the rising edge unless you cut off power.


- Stores data bits
- For most of time acts as barrier between input and output
- As C rises, loads input
- So you'd better compute the input before the C signal rises if you want to store the input data to the register

Clock Signal

 

- A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer


Clock Signal

 


- A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer




Clock Signal

 

 
- A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer



Clock Signal

 


 - A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer




Clock Signal

 - Cycle time of a clock signal: the time duration between two rising edges.




Clock Signal

 - Cycle time of a clock signal: the time duration between two rising edges.




Clock Signal

 - Cycle time of a clock signal: the time duration between two rising edges.
- Frequency of a clock signal: how many rising (falling) edges in 1 second.




Clock Signal

 - Cycle time of a clock signal: the time duration between two rising edges.
- Frequency of a clock signal: how many rising (falling) edges in 1 second.
- 1 GHz CPU means the clock frequency is 1 GHz



Clock Signal

 
- Cycle time of a clock signal: the time duration between two rising edges.
- Frequency of a clock signal: how many rising (falling) edges in 1 second.
- 1 GHz CPU means the clock frequency is 1 GHz
 - The cycle time is $1/10^9 = 1 \text{ ns}$



Register File

- A register file consists of a set of registers that you can individual read from and write to.


Register File

 

Register File


- A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out

Register File

 


Register File

 - A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out




Register File

 - A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out




Register File

 - A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out




Register File

 - A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out
- To write: give a register file ID, a new value, overwrite the old value




Register File

 - A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out
- To write: give a register file ID, a new value, overwrite the old value




Register File

 - A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out
- To write: give a register file ID, a new value, overwrite the old value




Register File

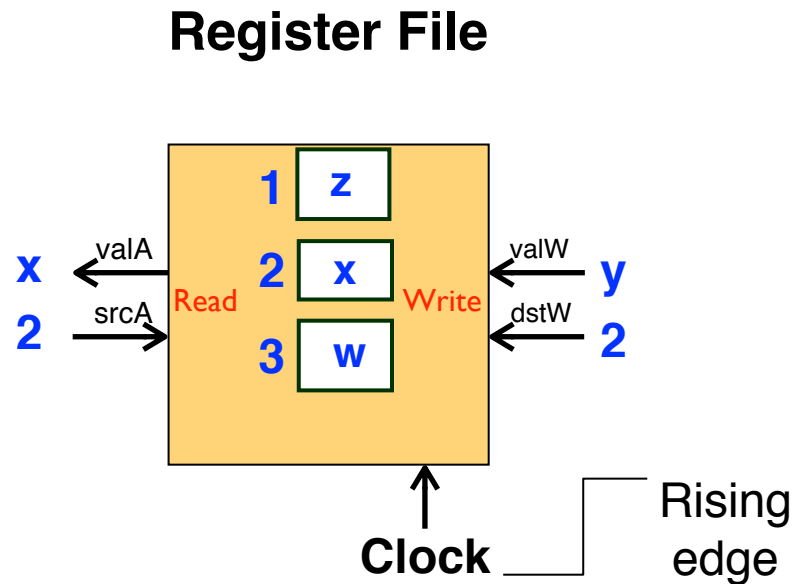- A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out
- To write: give a register file ID, a new value, overwrite the old value



Register File

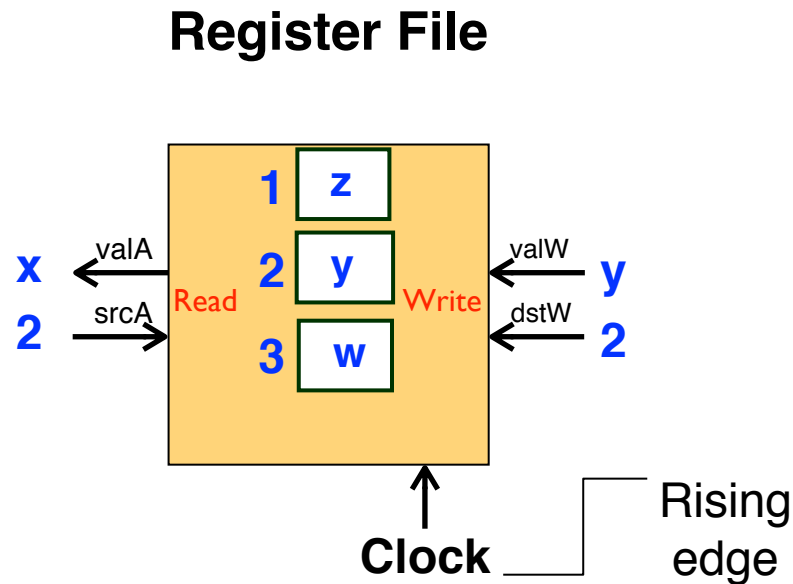
- A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out
- To write: give a register file ID, a new value, overwrite the old value



Register File


- A register file consists of a set of registers that you can individual read from and write to.
- To read: give a register file ID, and read the stored value out
- To write: give a register file ID, a new value, overwrite the old value
- How do we build a register file out of individual registers??

Register File

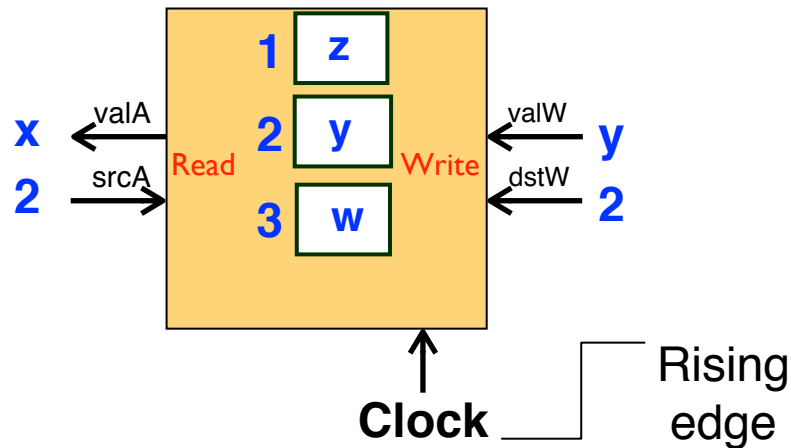


Register File Read

 - Continuously read a register independent of the clock signal




Register File Read

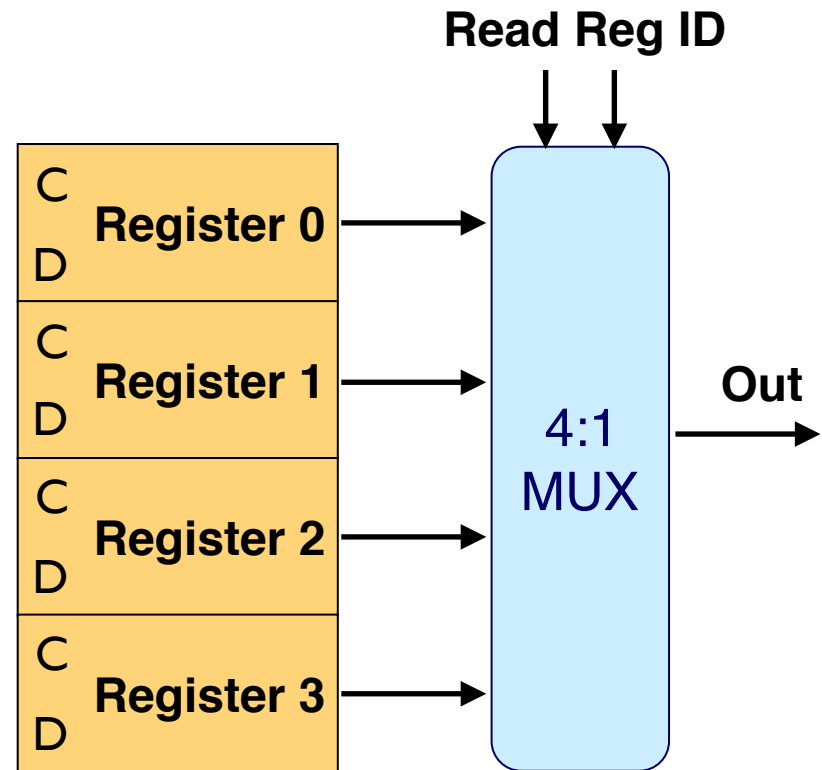
- Continuously read a register independent of the clock signal




Register File Write

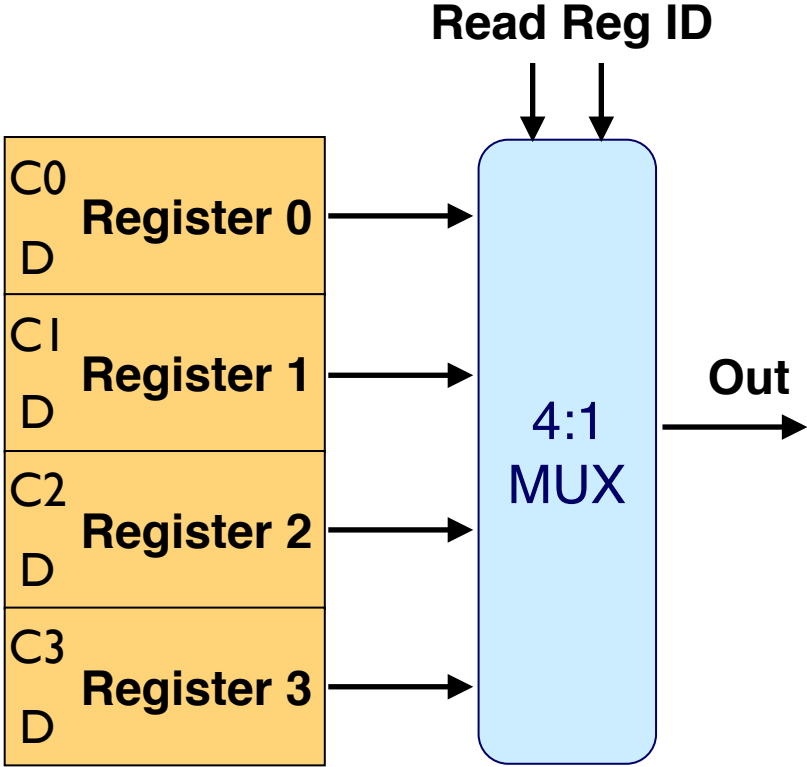

Register File Write

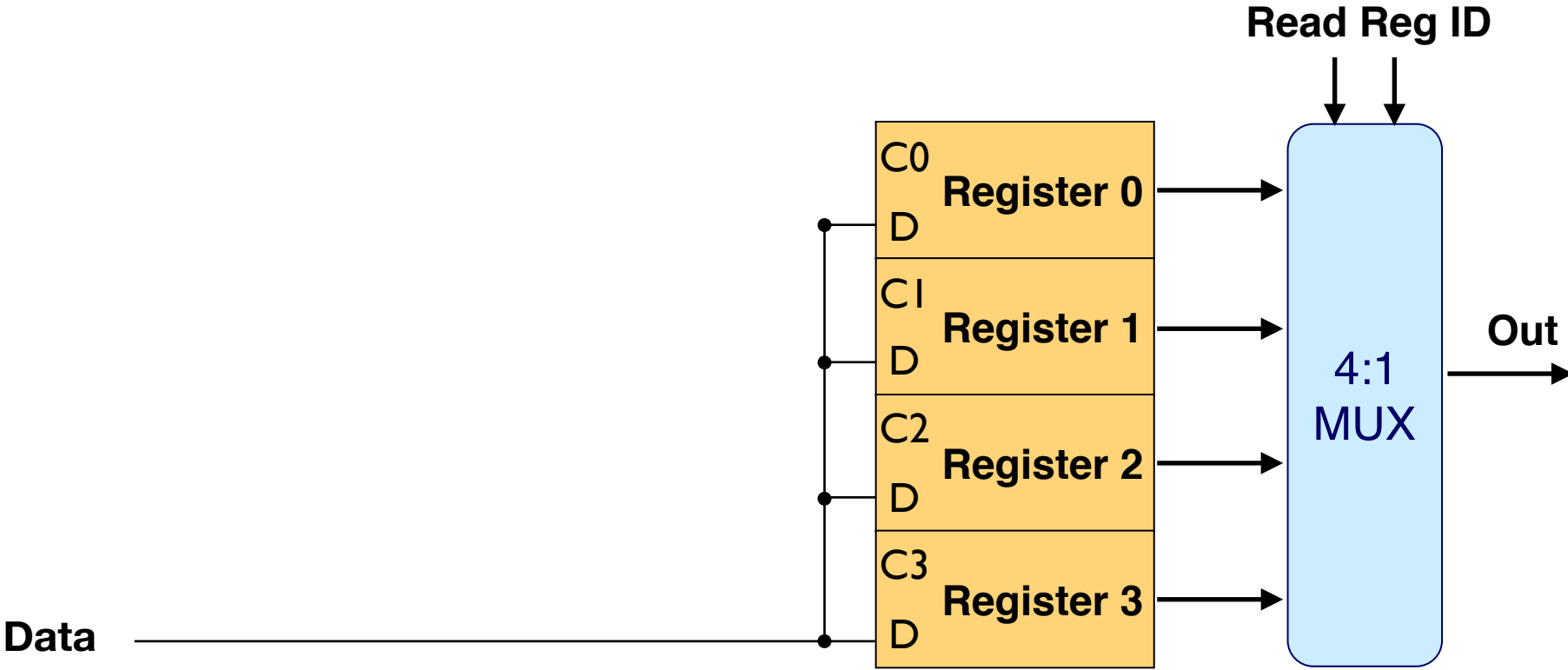


Register File Write

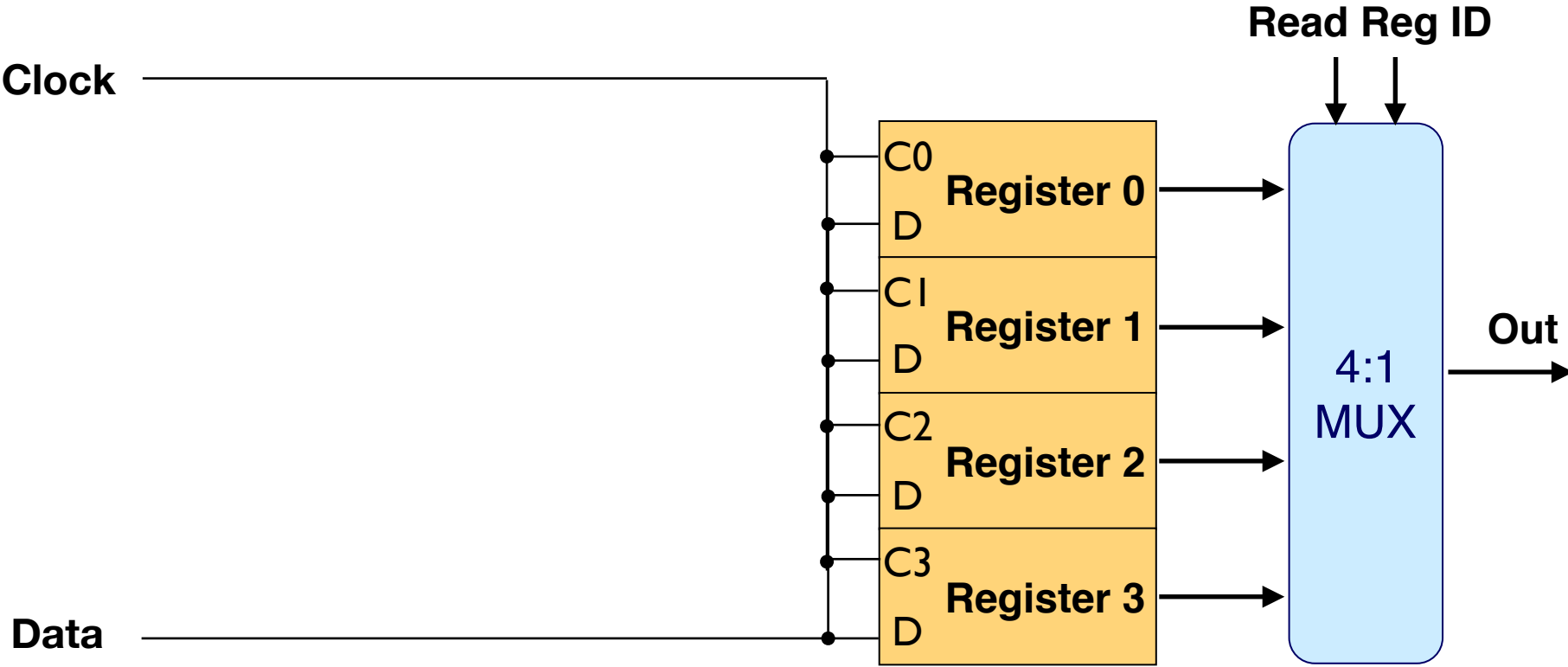


Register File Write

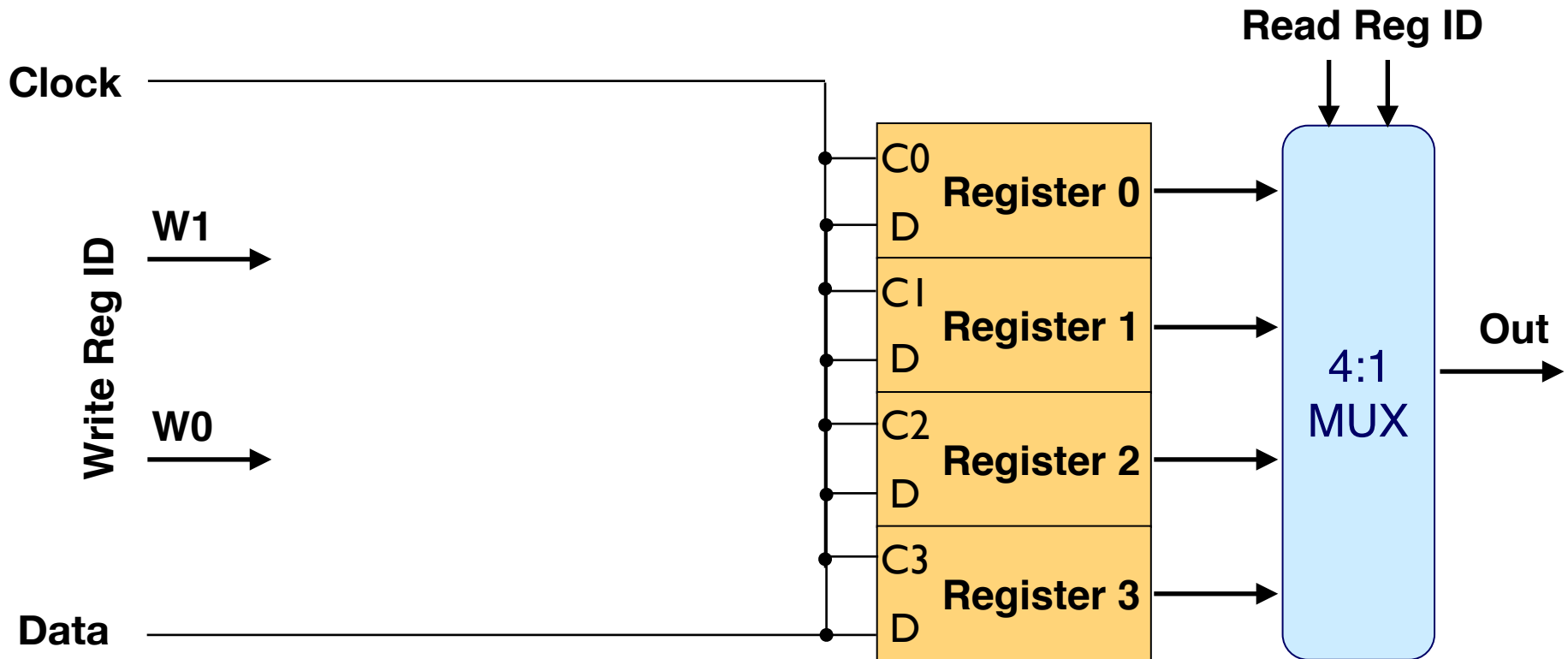- Only write the a specific register when the clock rises. How??



Register File Write

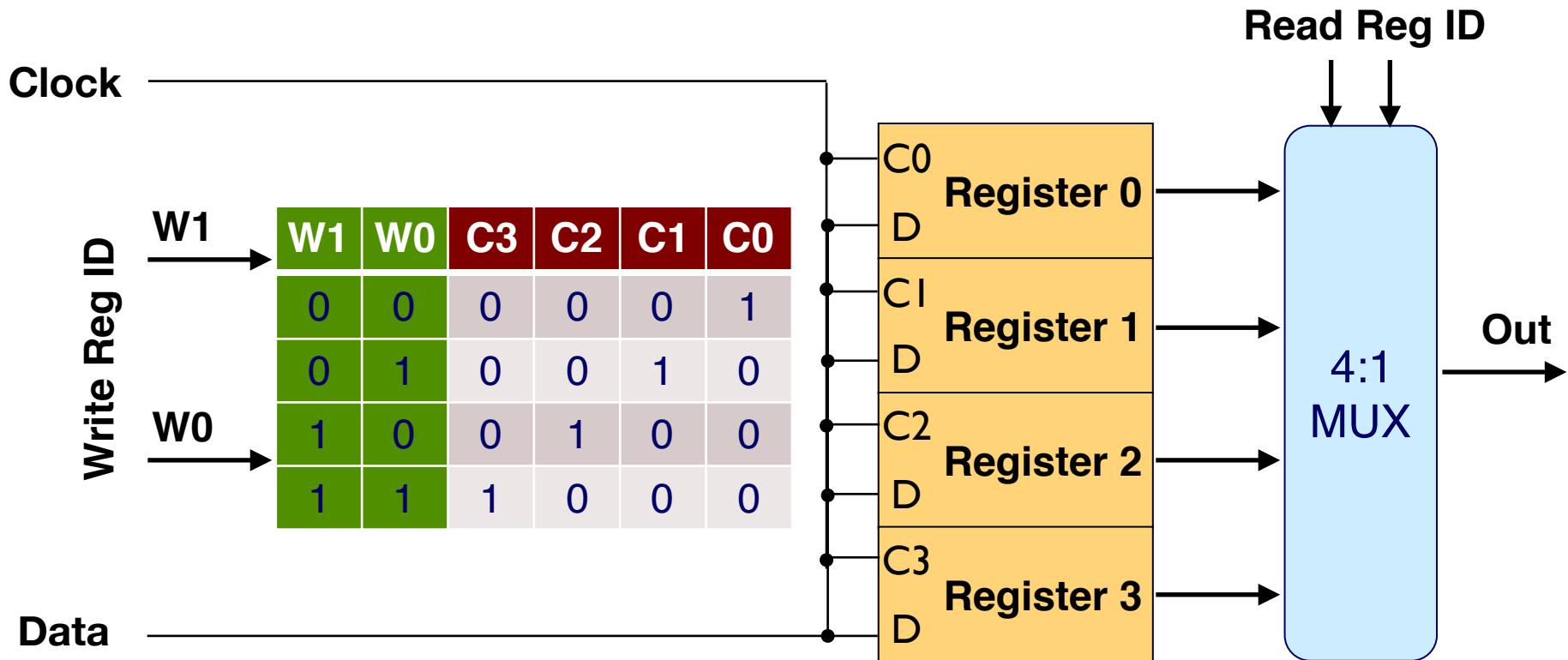- Only write the a specific register when the clock rises. How??



Decoder

W1	W0	C3	C2	C1	C0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

W0 _

W1 _

_C0

_C1

_C2

_C3

Decoder

W1	W0	C3	C2	C1	C0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

W0 _

W1 _

_C0

_C1

_C2

_C3

$$C0 = !W1 \& !W0$$

$$C1 = !W1 \& W0$$

$$C2 = W1 \& !W0$$

$$C3 = W1 \& W0$$

Decoder


W1	W0	C3	C2	C1	C0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

$$C0 = !W1 \& !W0$$


$$C1 = !W1 \& W0$$

$$C2 = W1 \& !W0$$


$$C3 = W1 \& W0$$

 


Register File Write

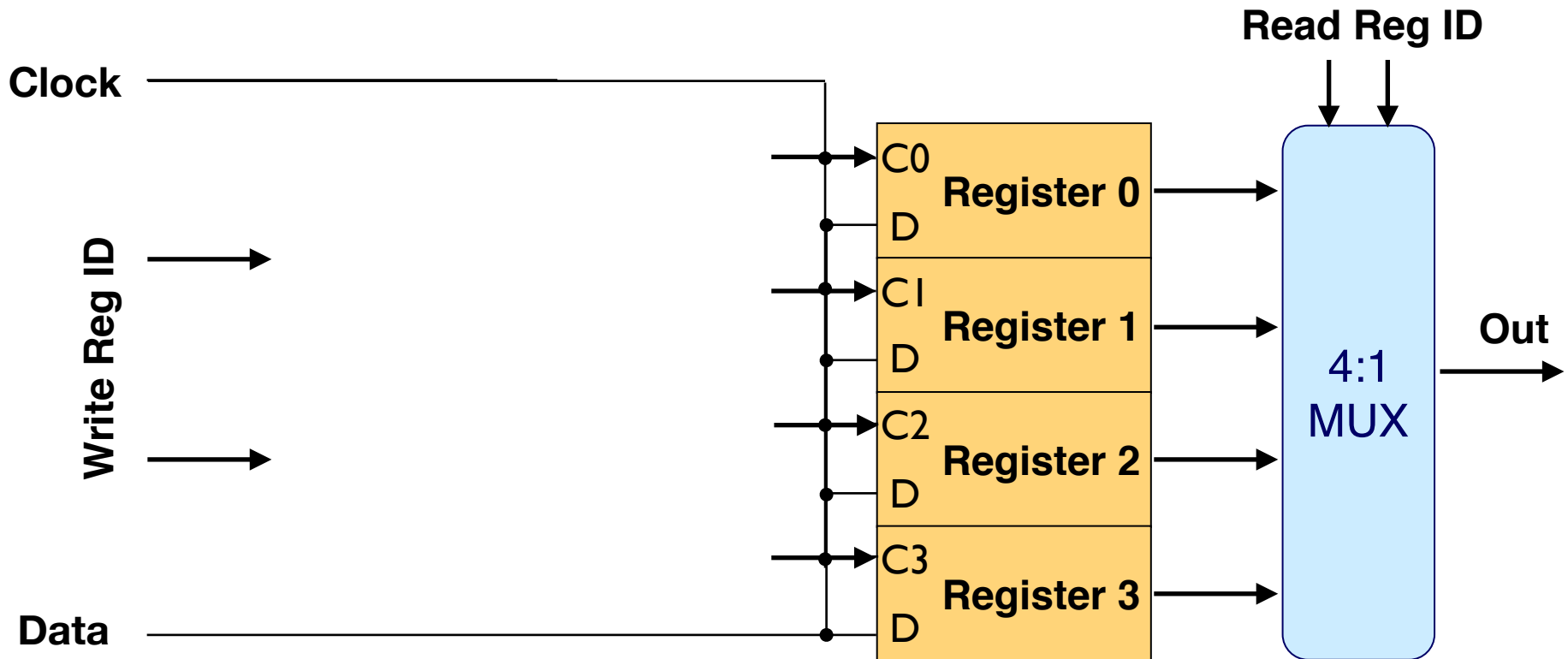


Register File Write

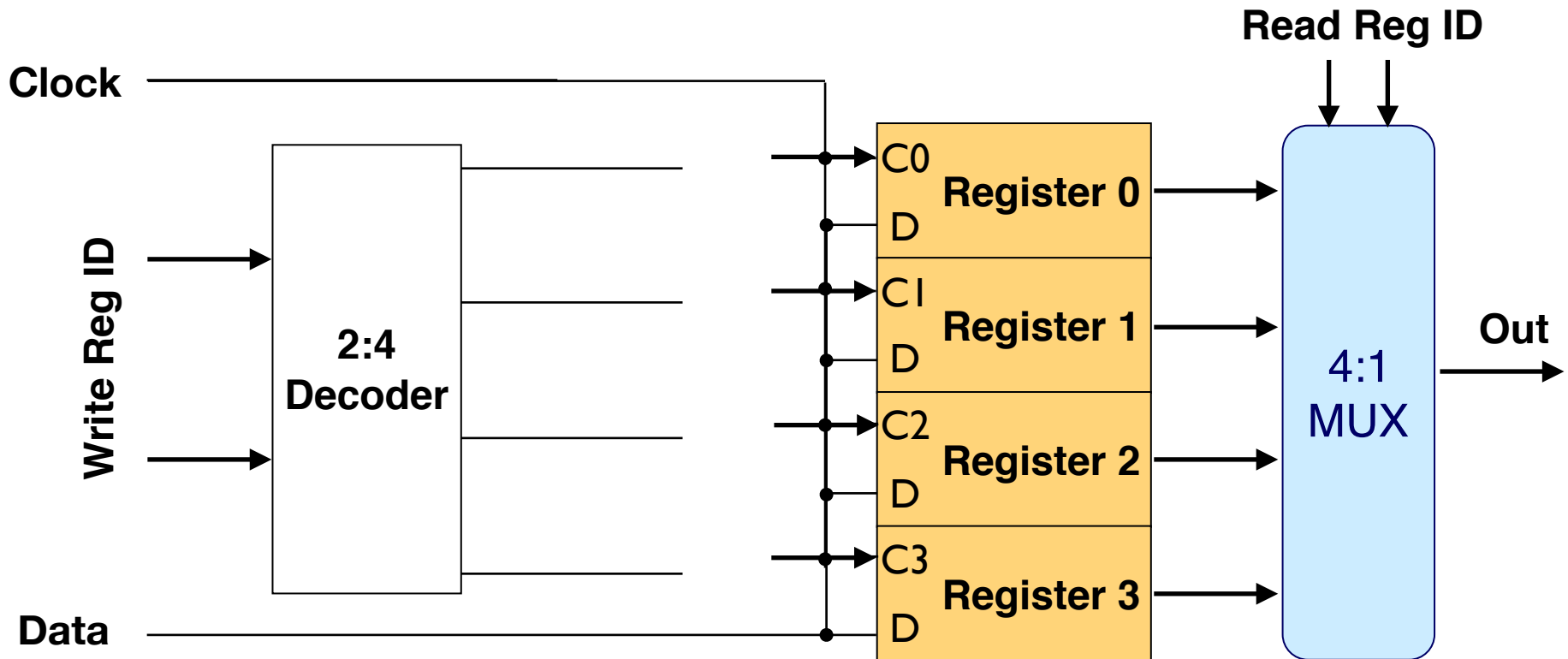


Register File Write

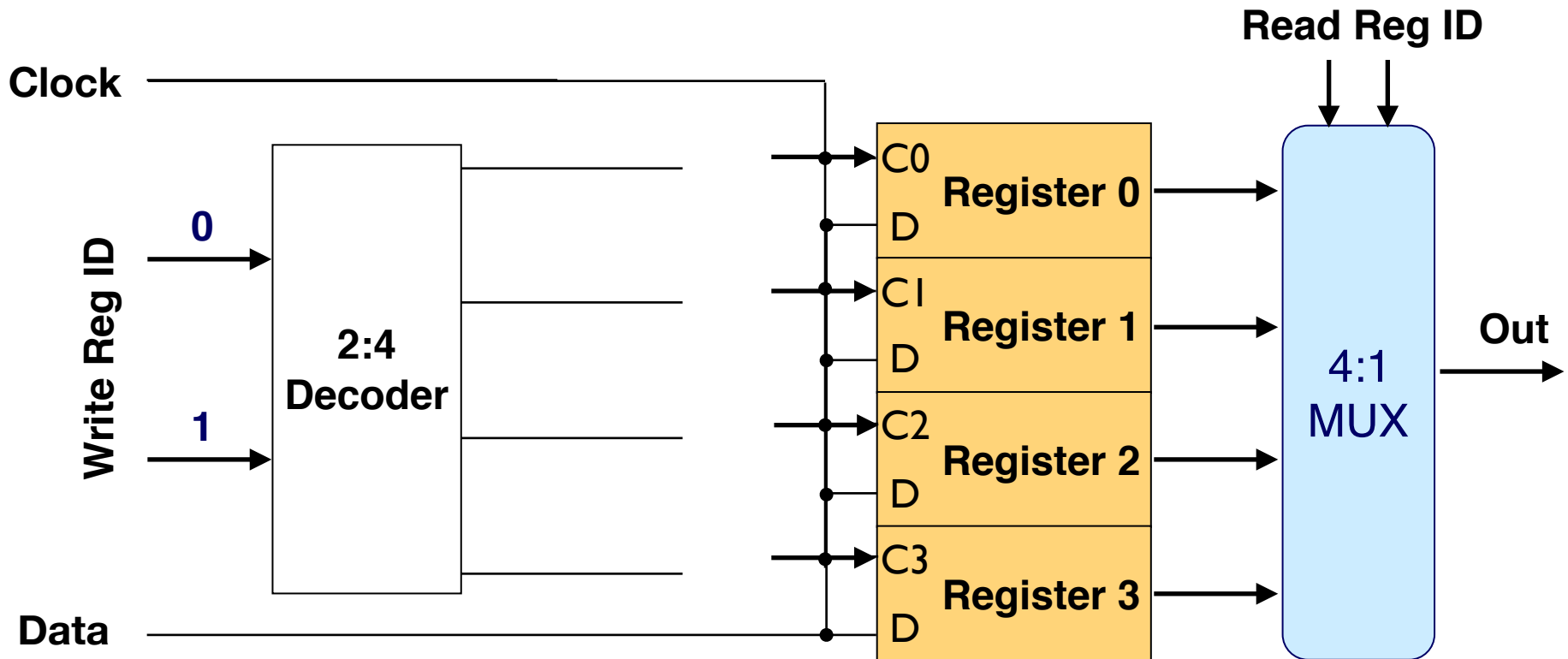


Register File Write

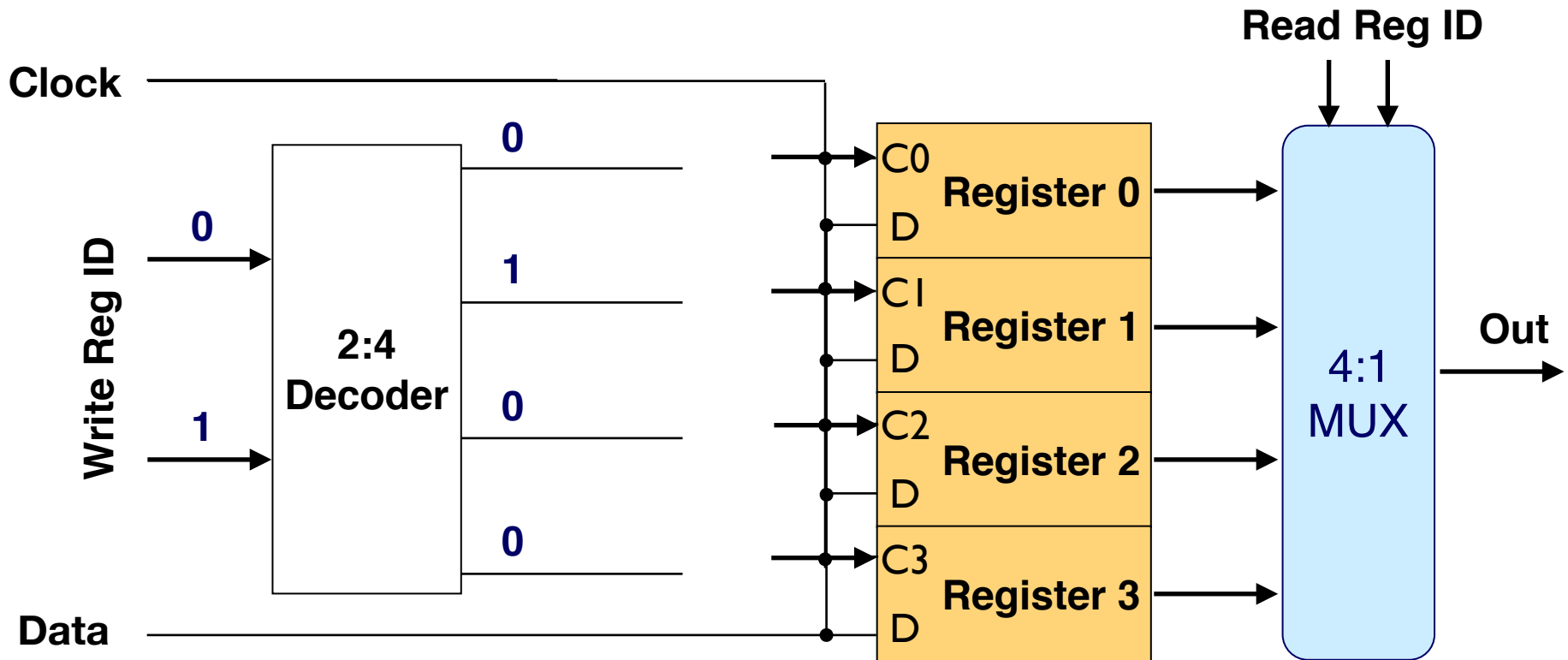

Register File Write

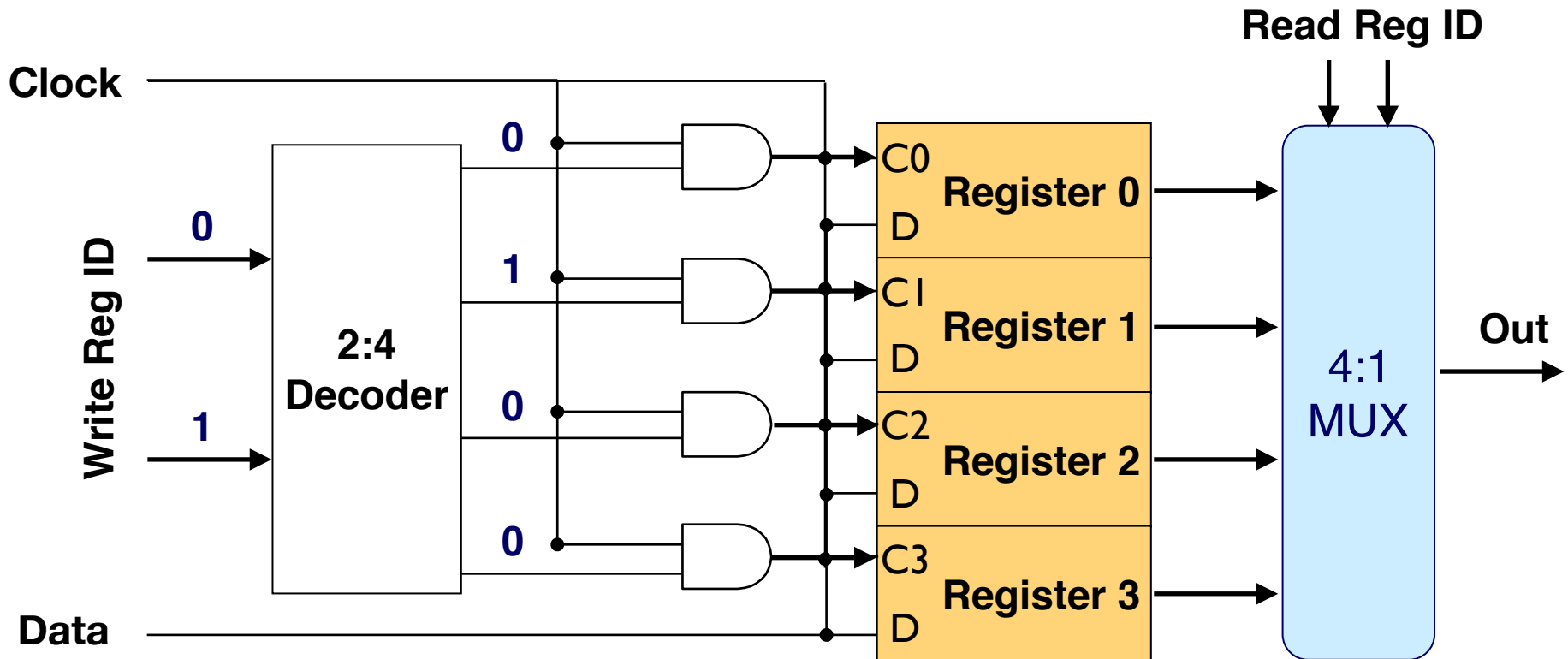


Register File Write

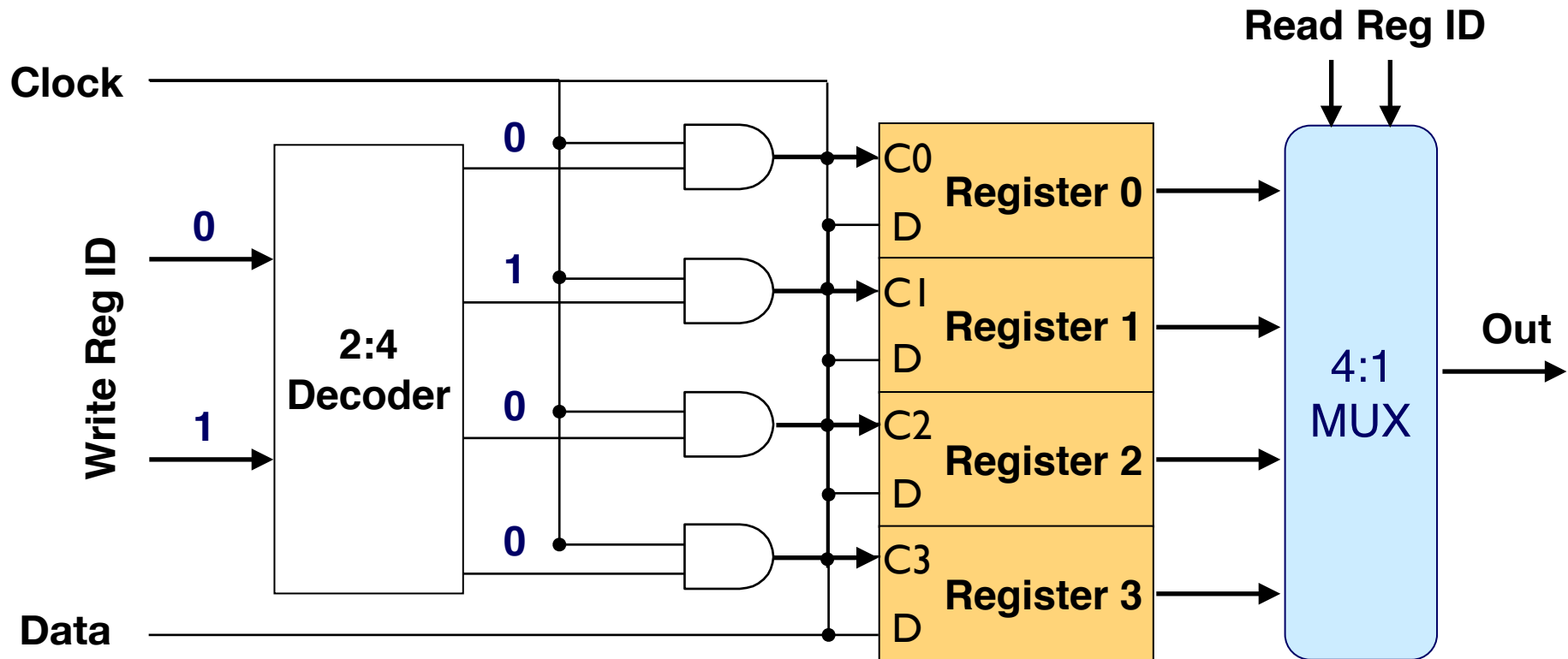

- This implementation can read 1 register and write 1 register at the same time: 1 read port and 1 write port


Multi-Port Register File

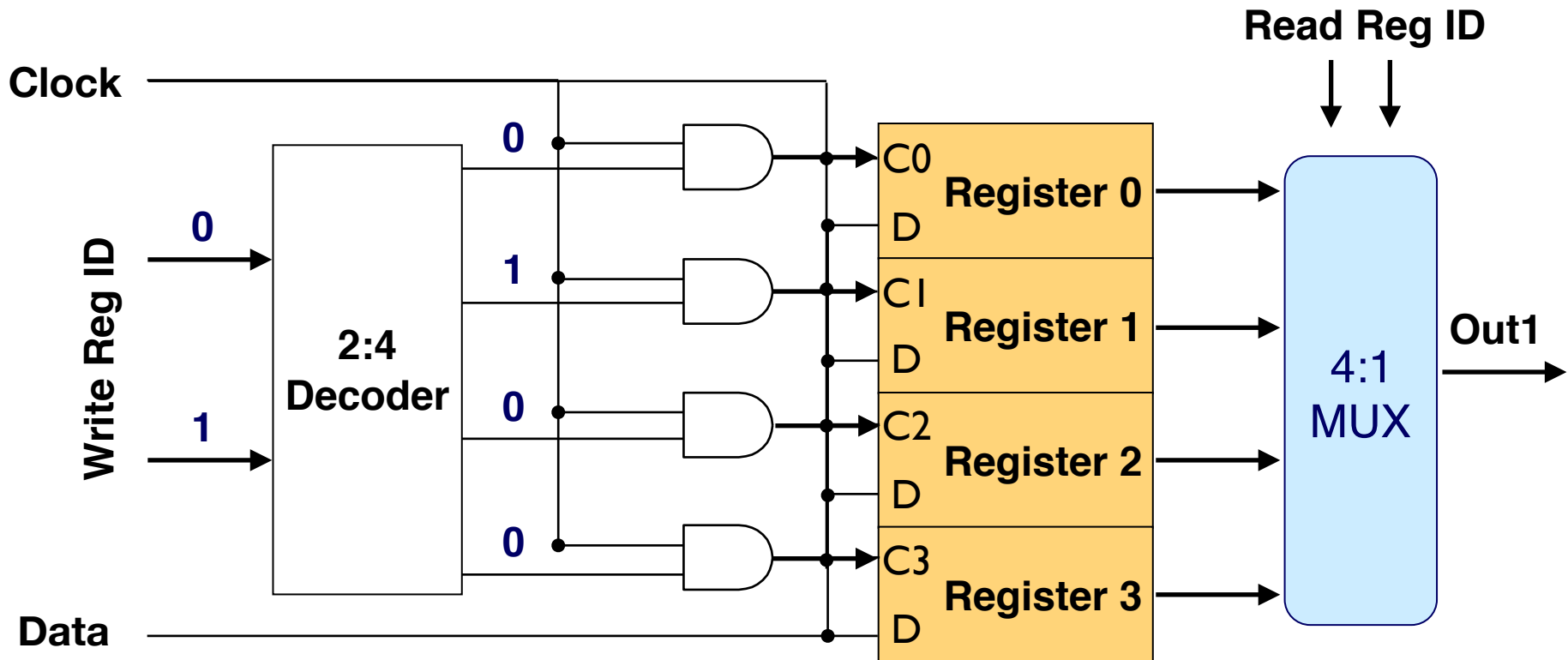- What if we want to read multiple registers at the same time?




Multi-Port Register File

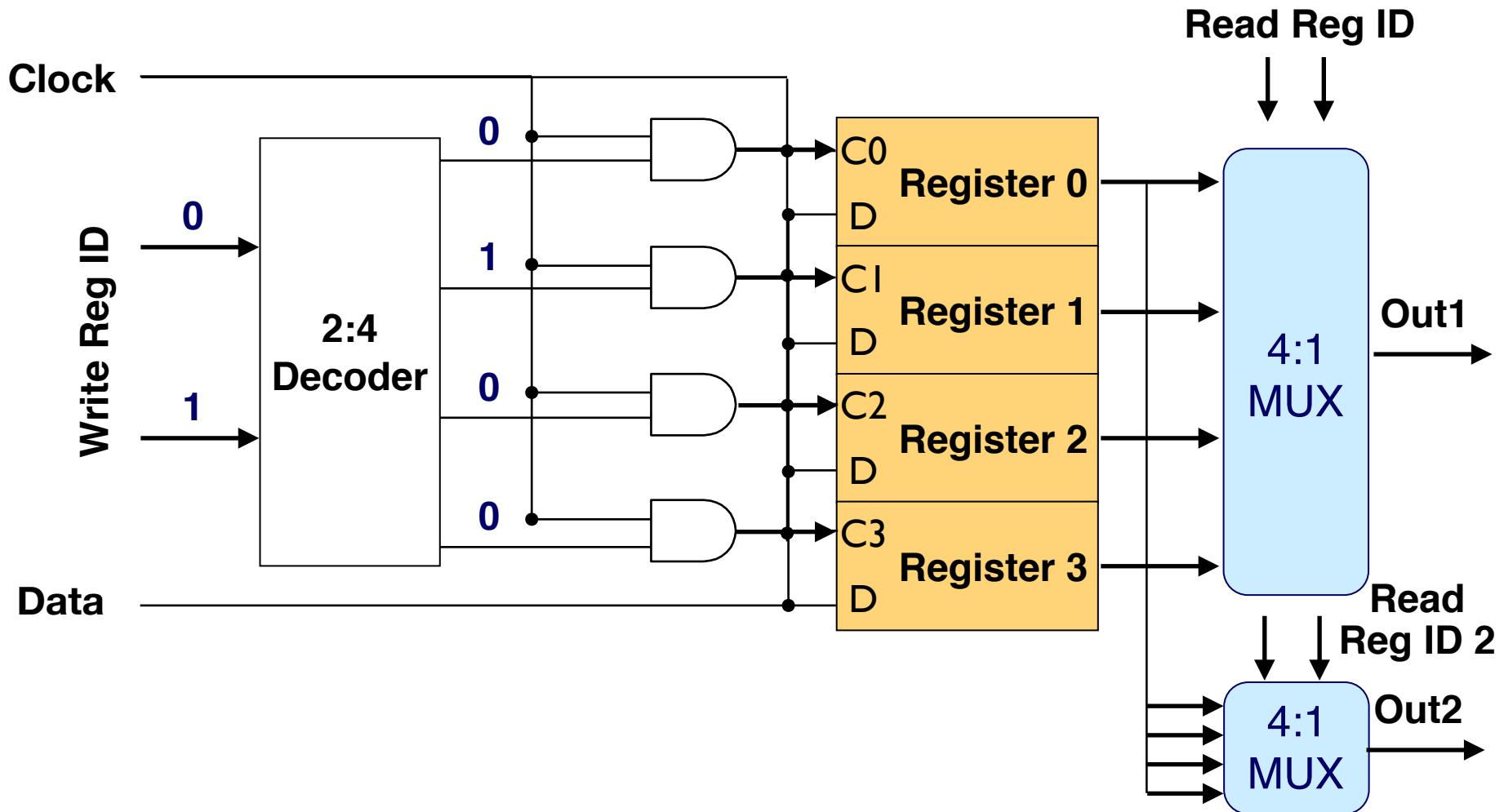- What if we want to read multiple registers at the same time?



Multi-Port Register File

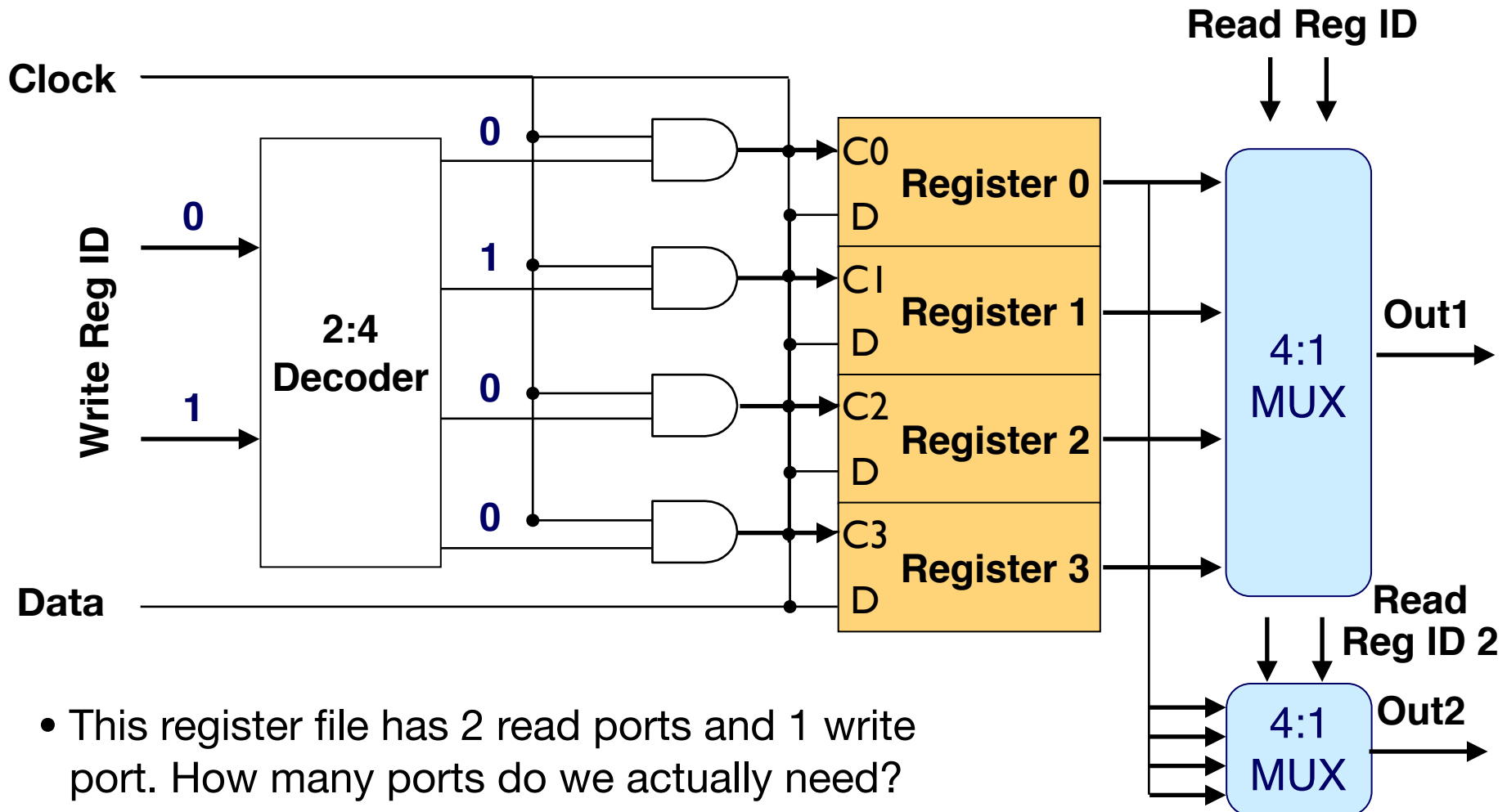
- What if we want to read multiple registers at the same time?



- This register file has 2 read ports and 1 write port. How many ports do we actually need?


Multi-Port Register File

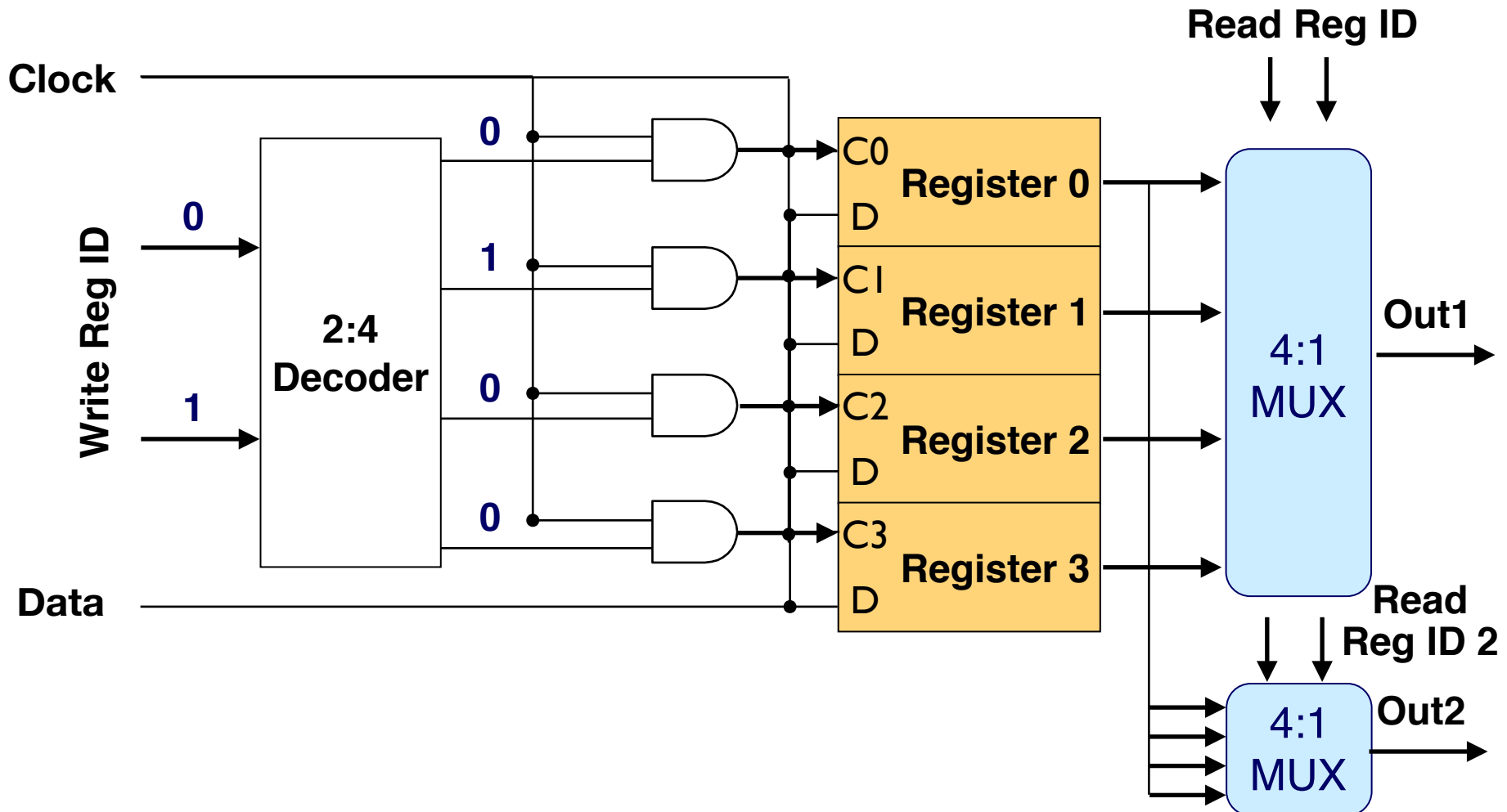- Is this correct? What if we don't want to write anything?




Multi-Port Register File

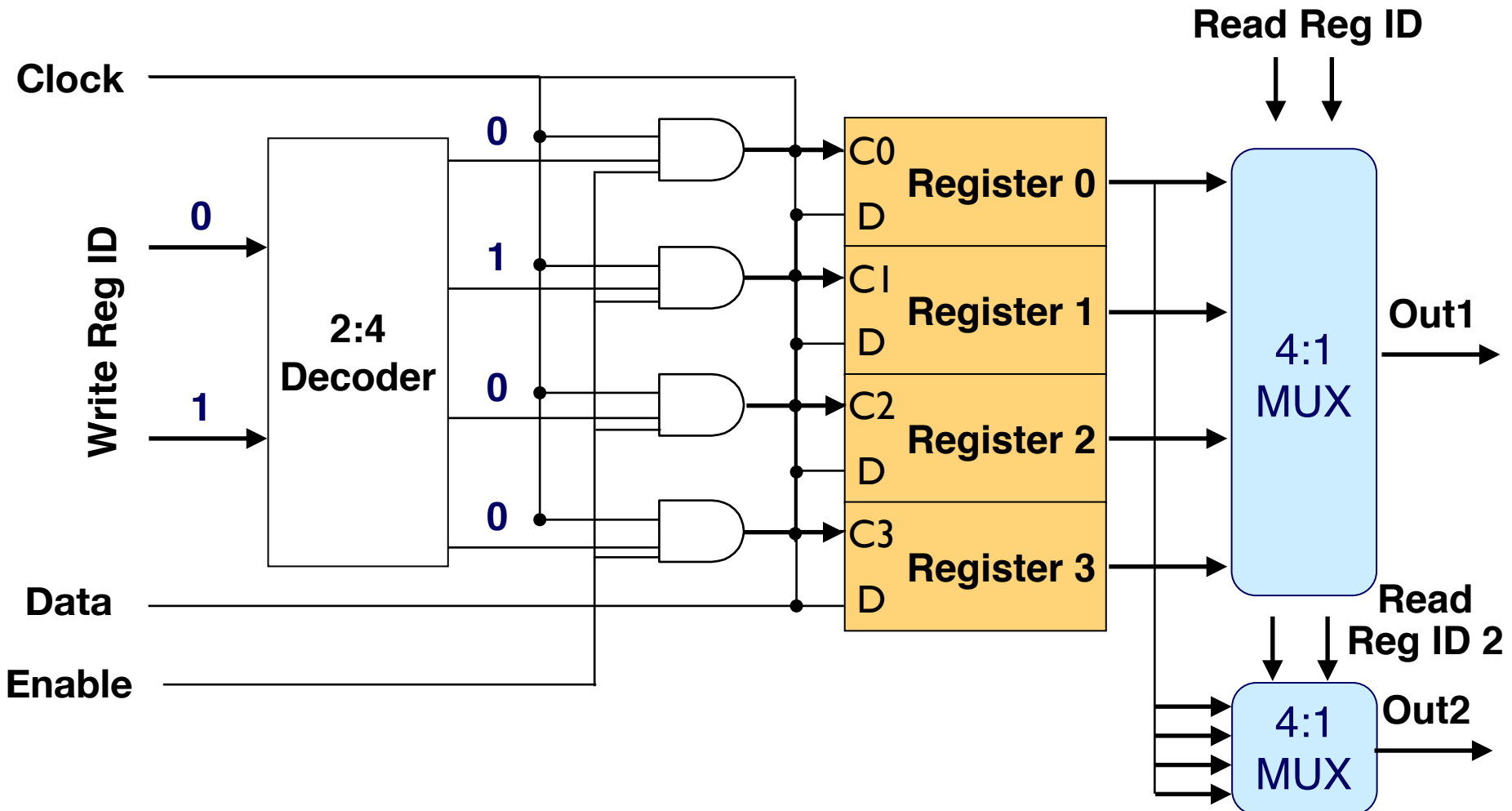- Is this correct? What if we don't want to write anything?





Executing an ADD instruction

 - How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`





Executing an ADD instruction

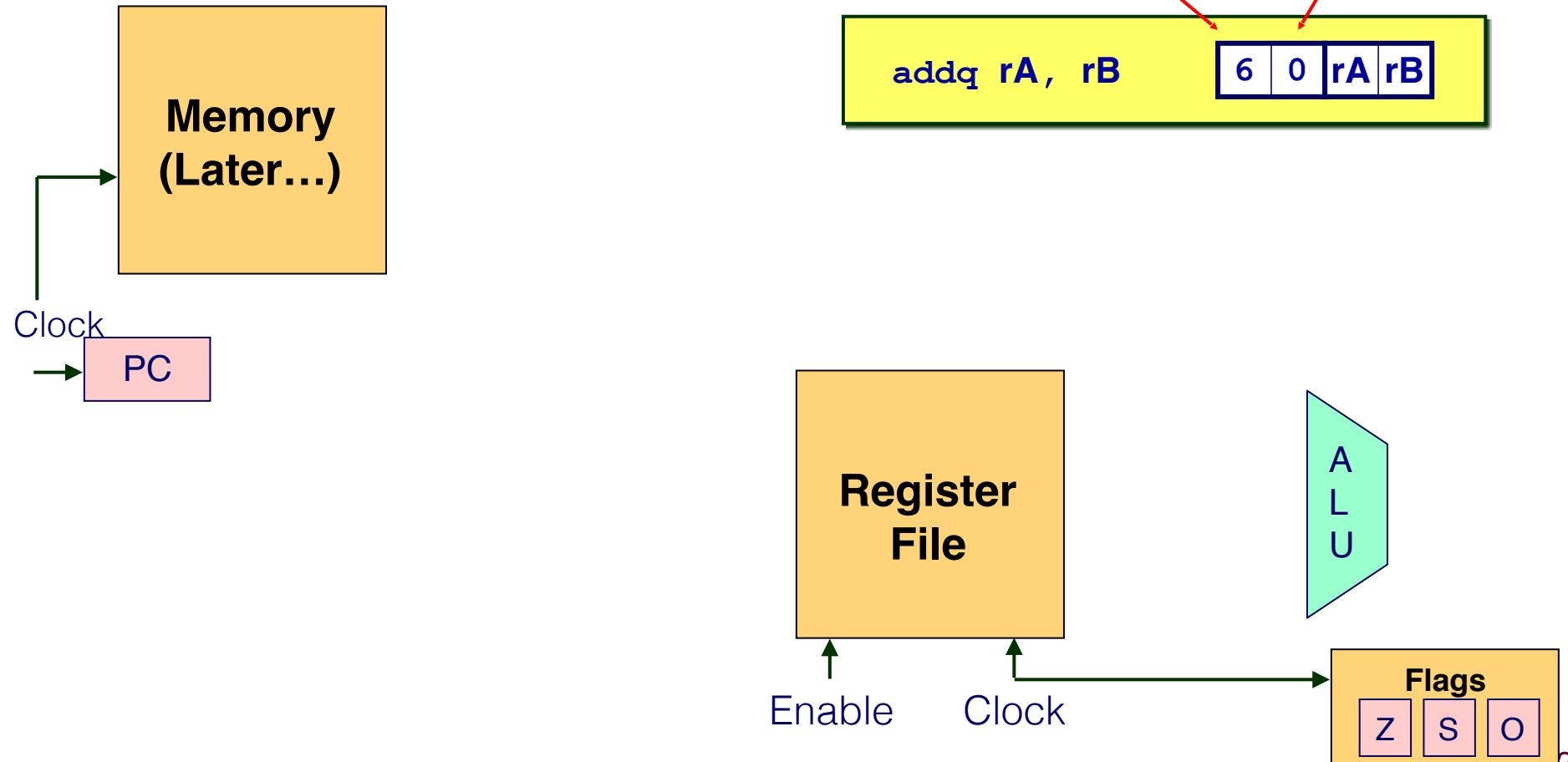 - How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`



Executing an ADD instruction

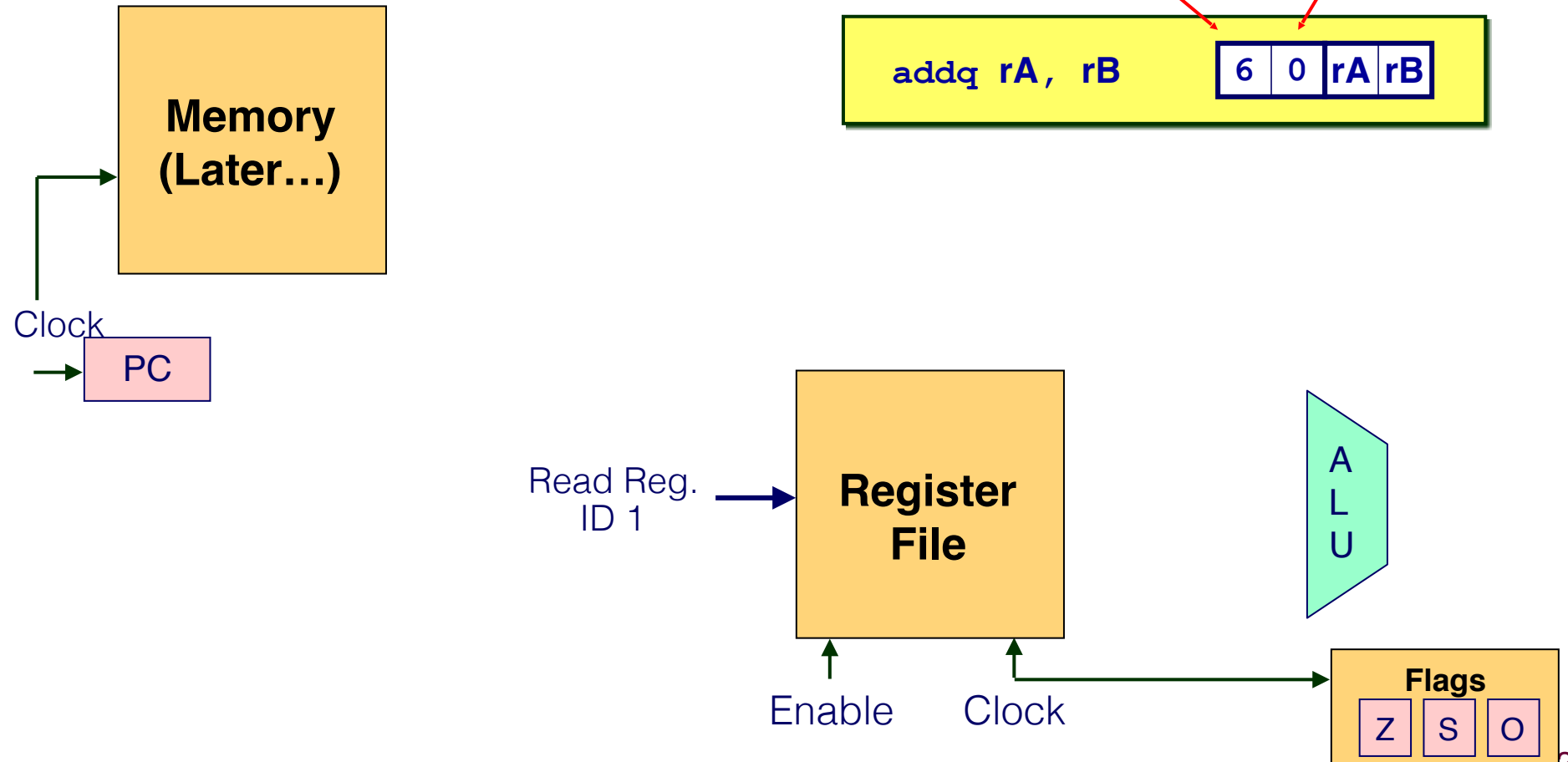 - How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`




Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`



Instruction Code
Add

Function Code

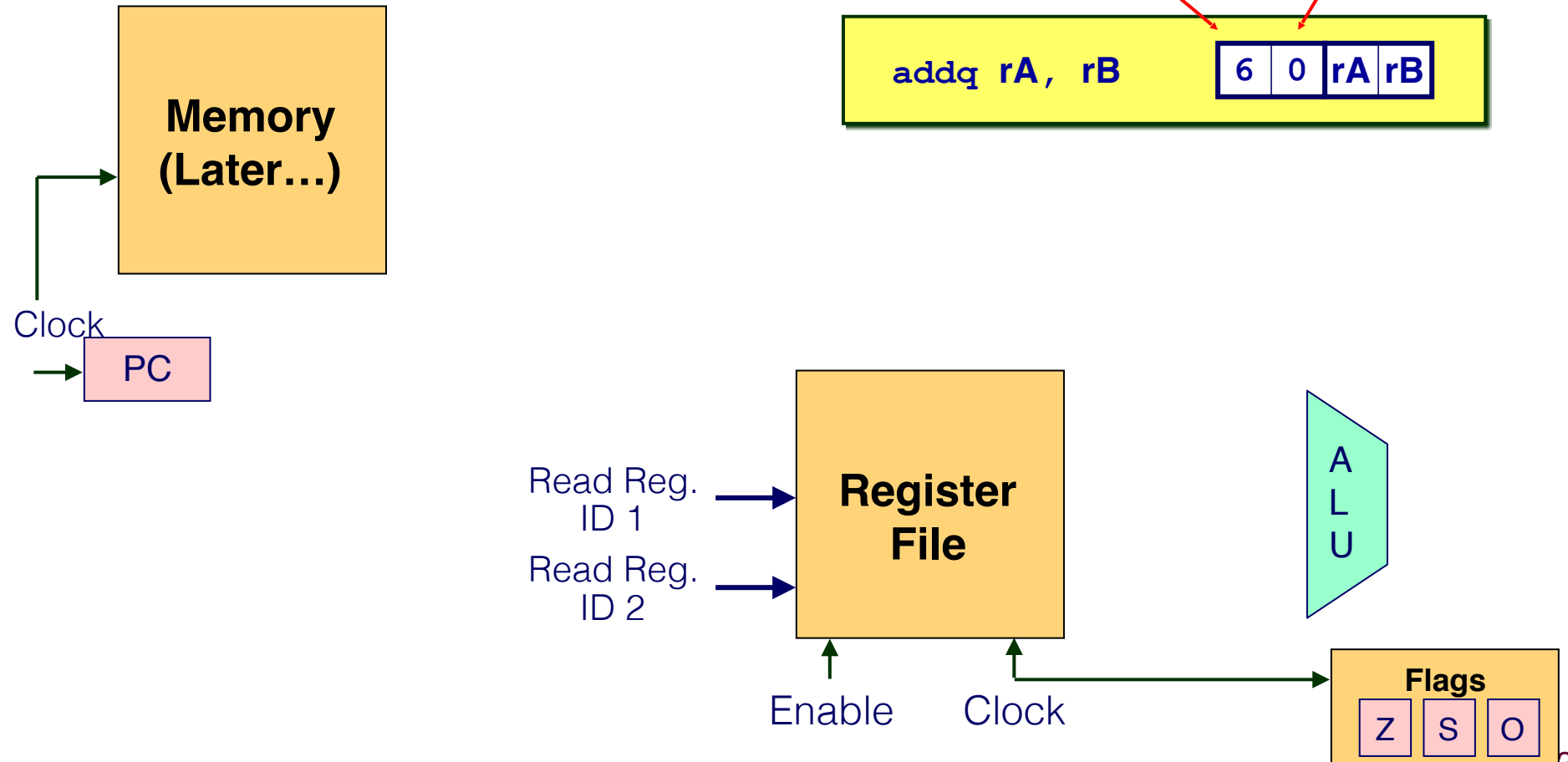

Executing an ADD instruction

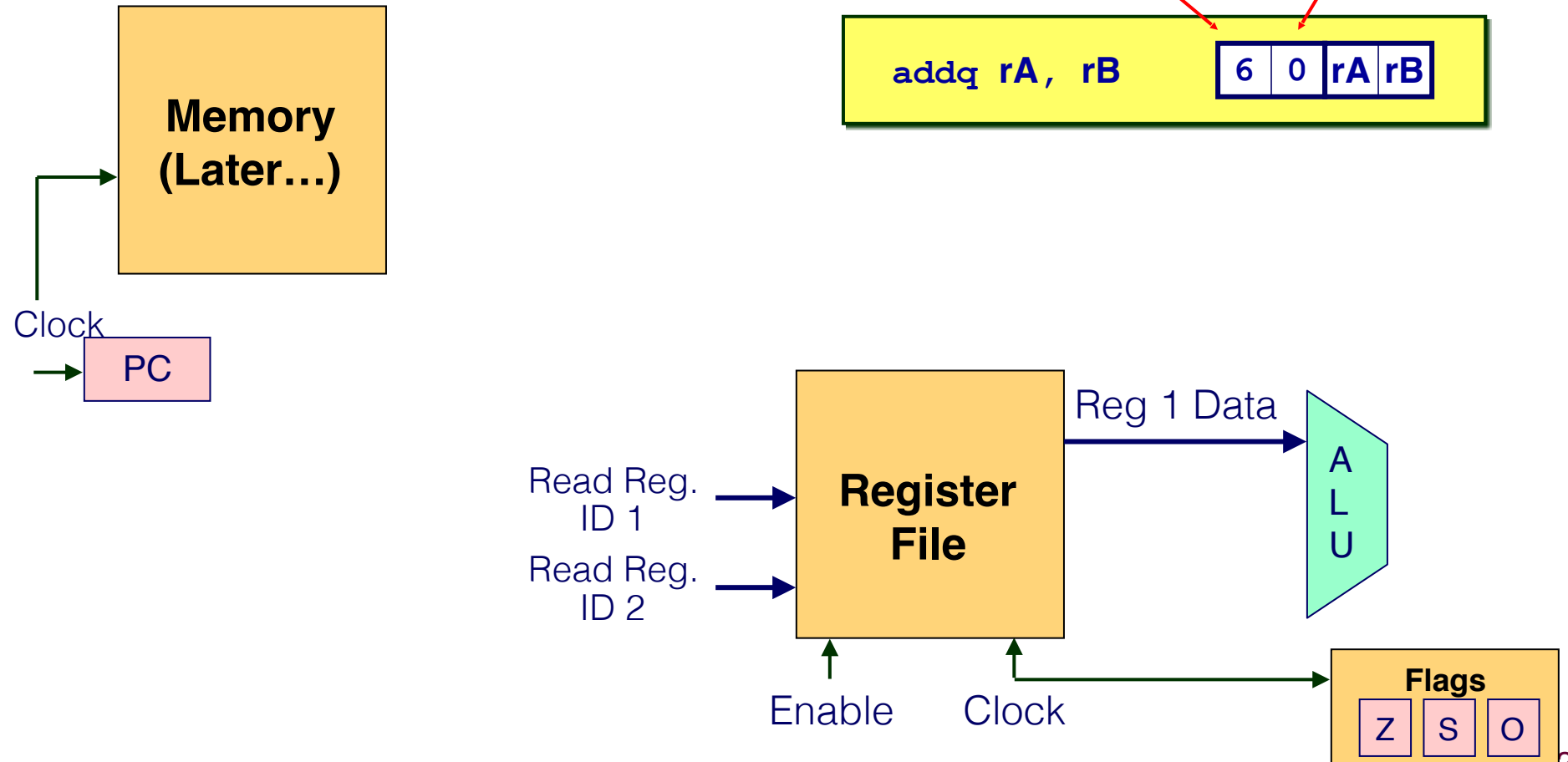 - How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`




Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`



Instruction Code
Add

Function Code

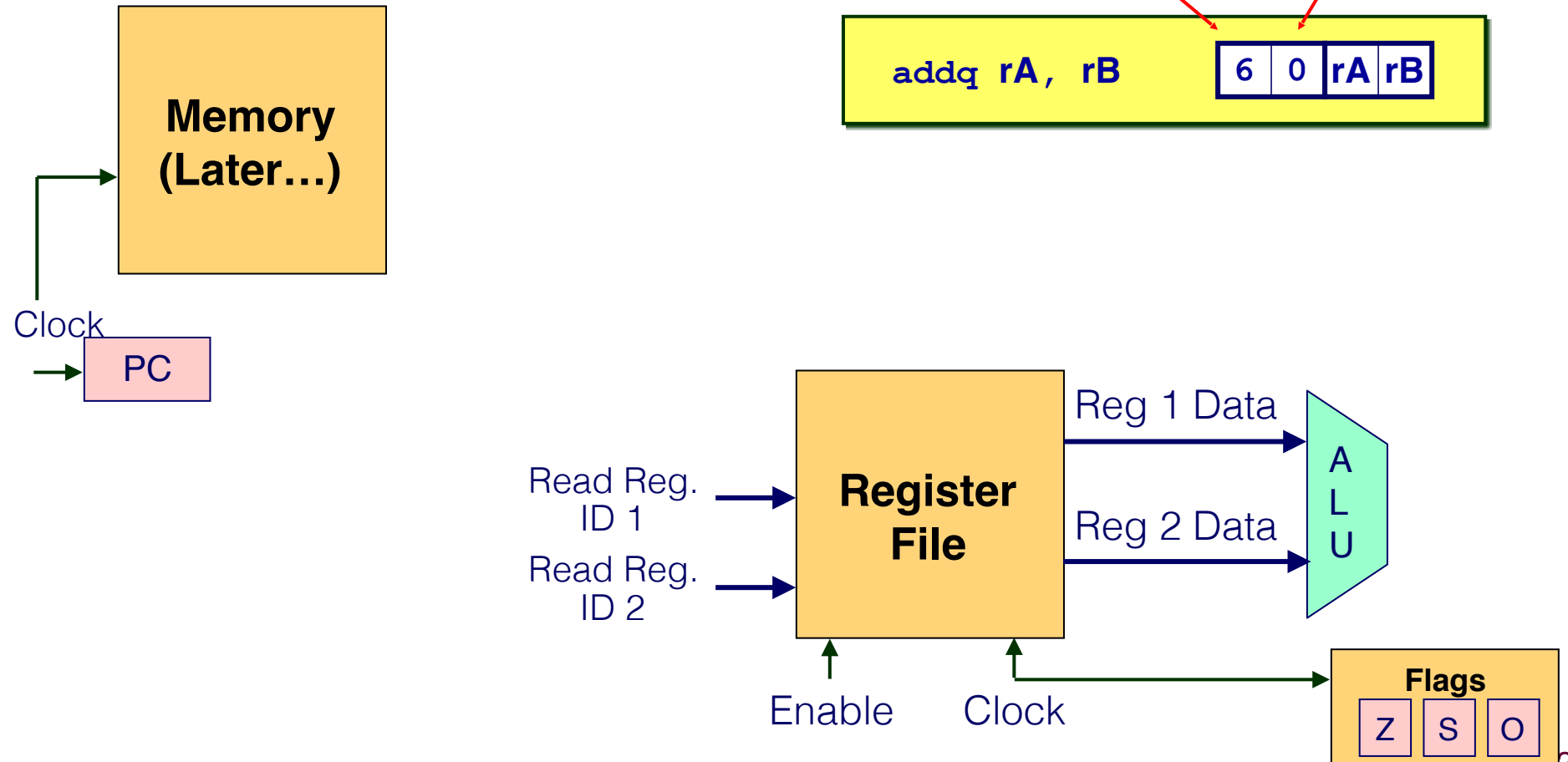

Executing an ADD instruction

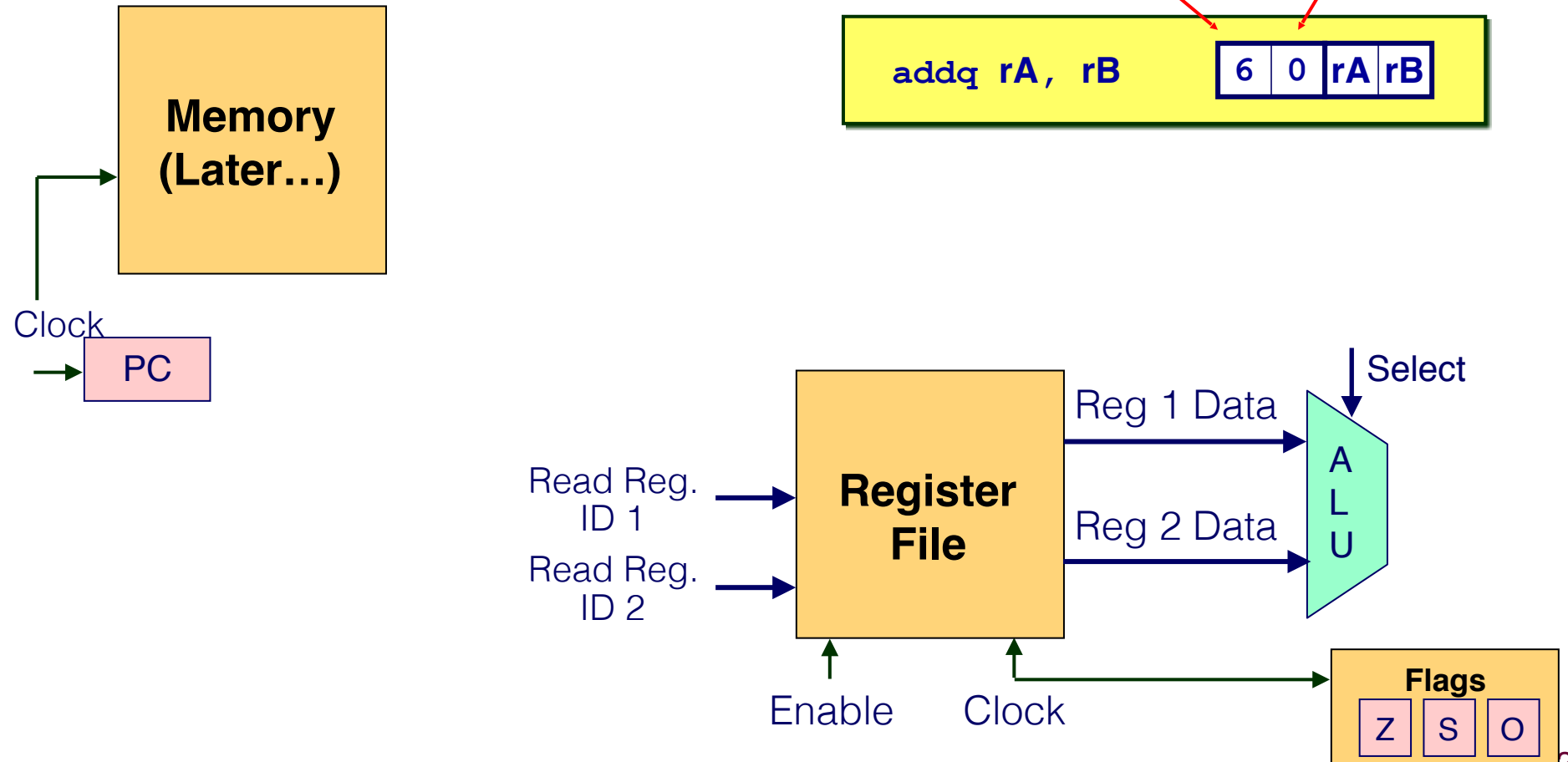 - How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`




Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`

Instruction Code
Add

Function Code

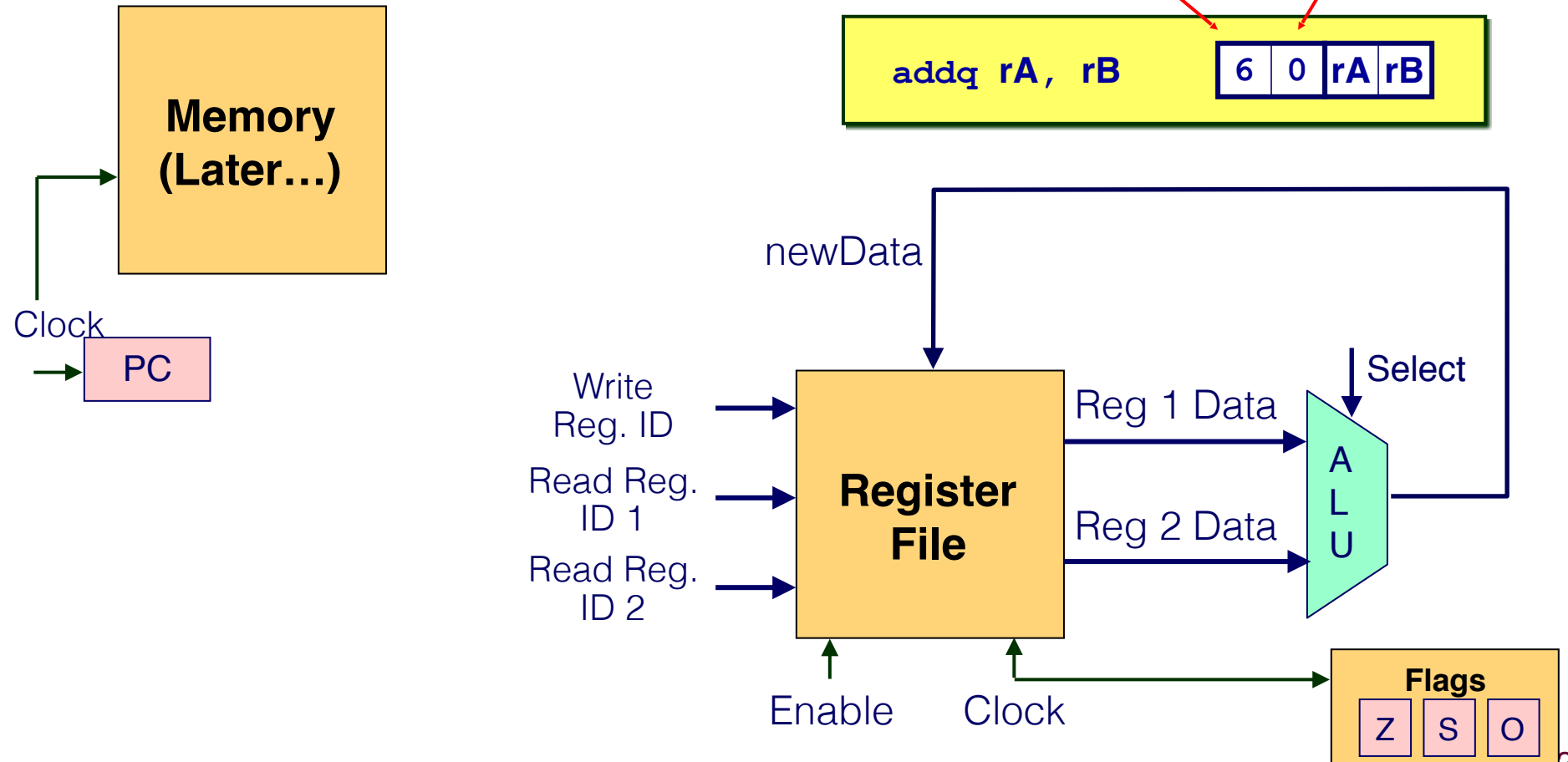


Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`

Instruction Code
Add


Function Code

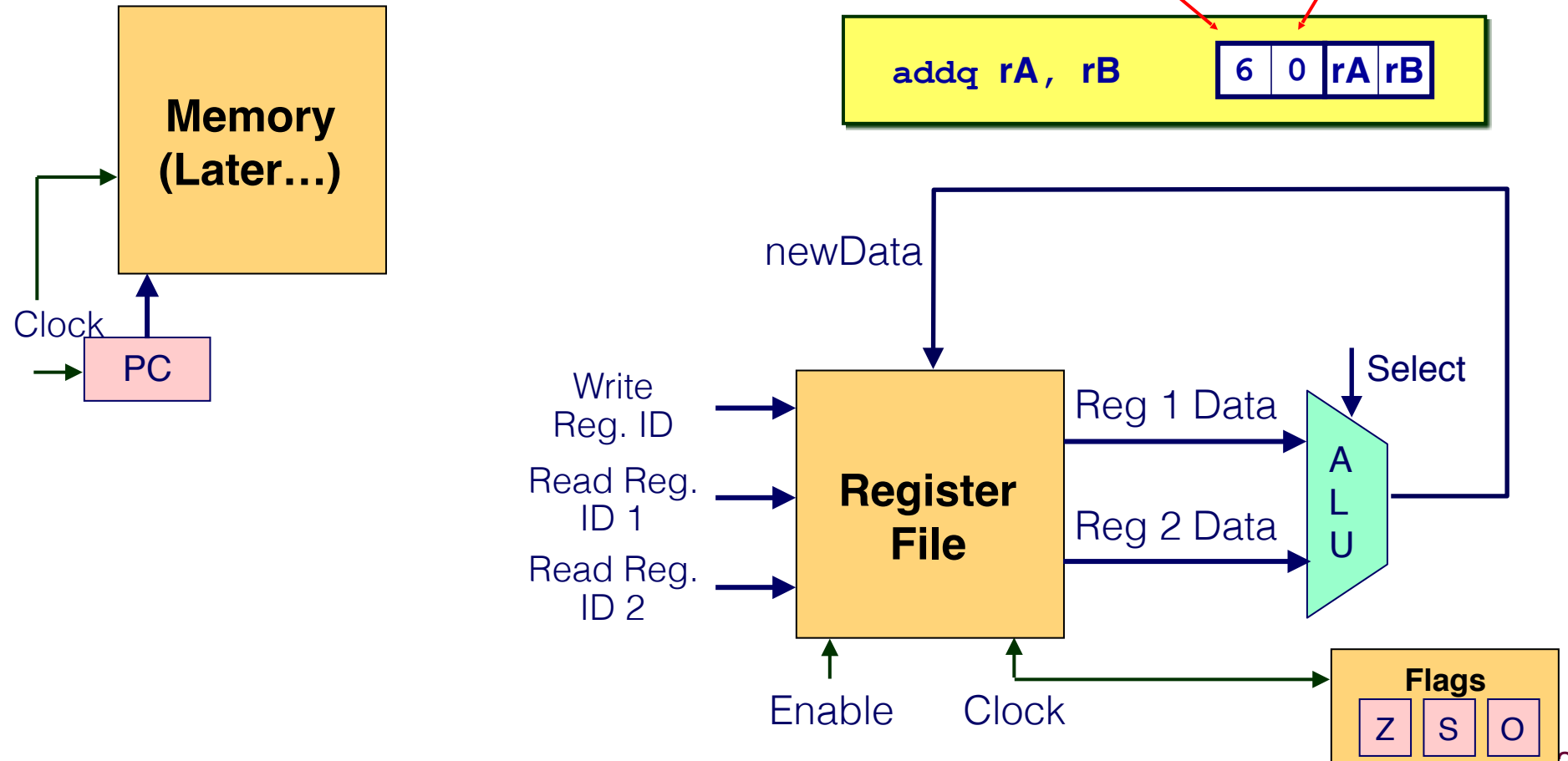

Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`


Instruction Code
Add

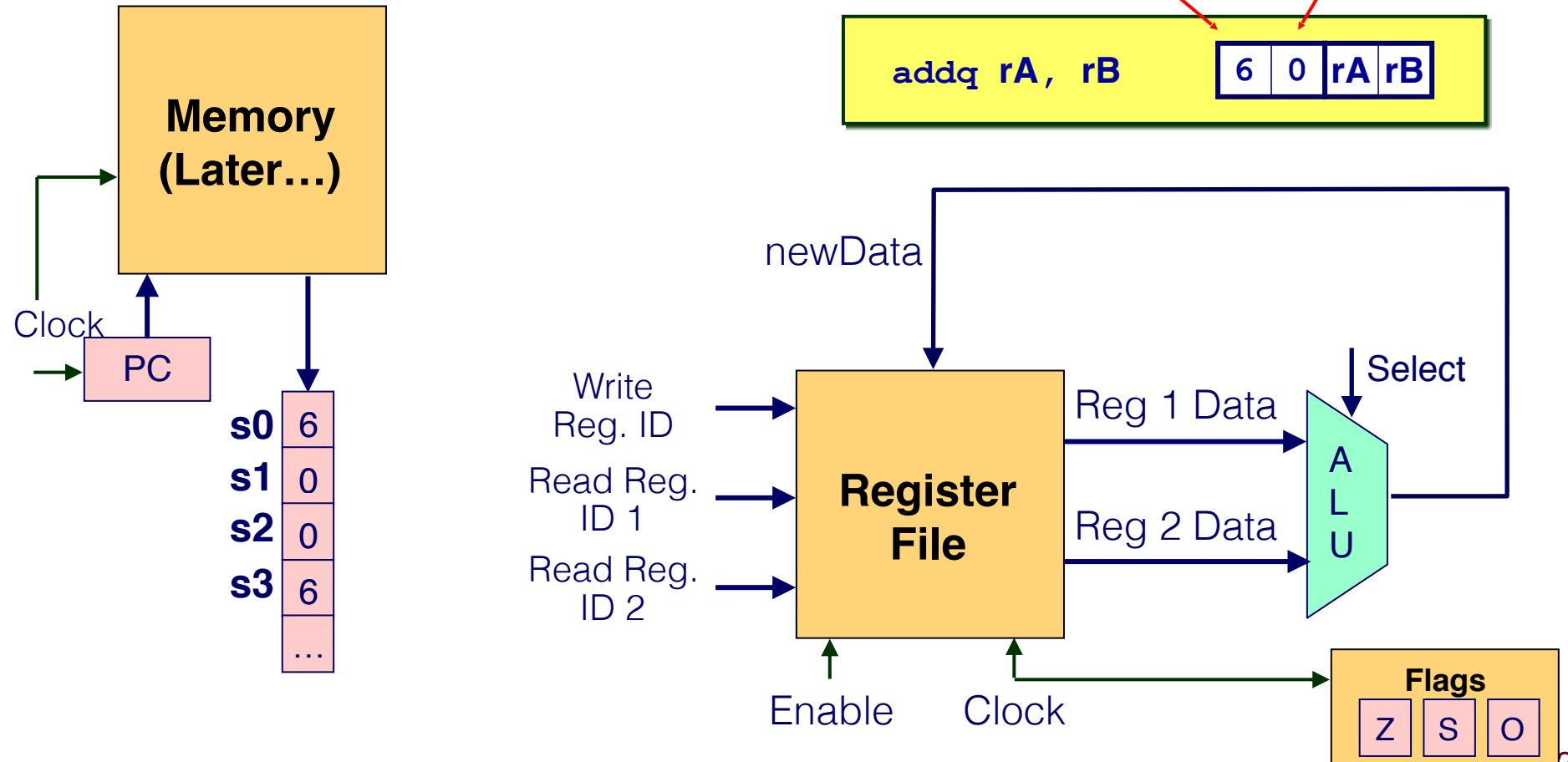

Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`


Instruction Code
Add

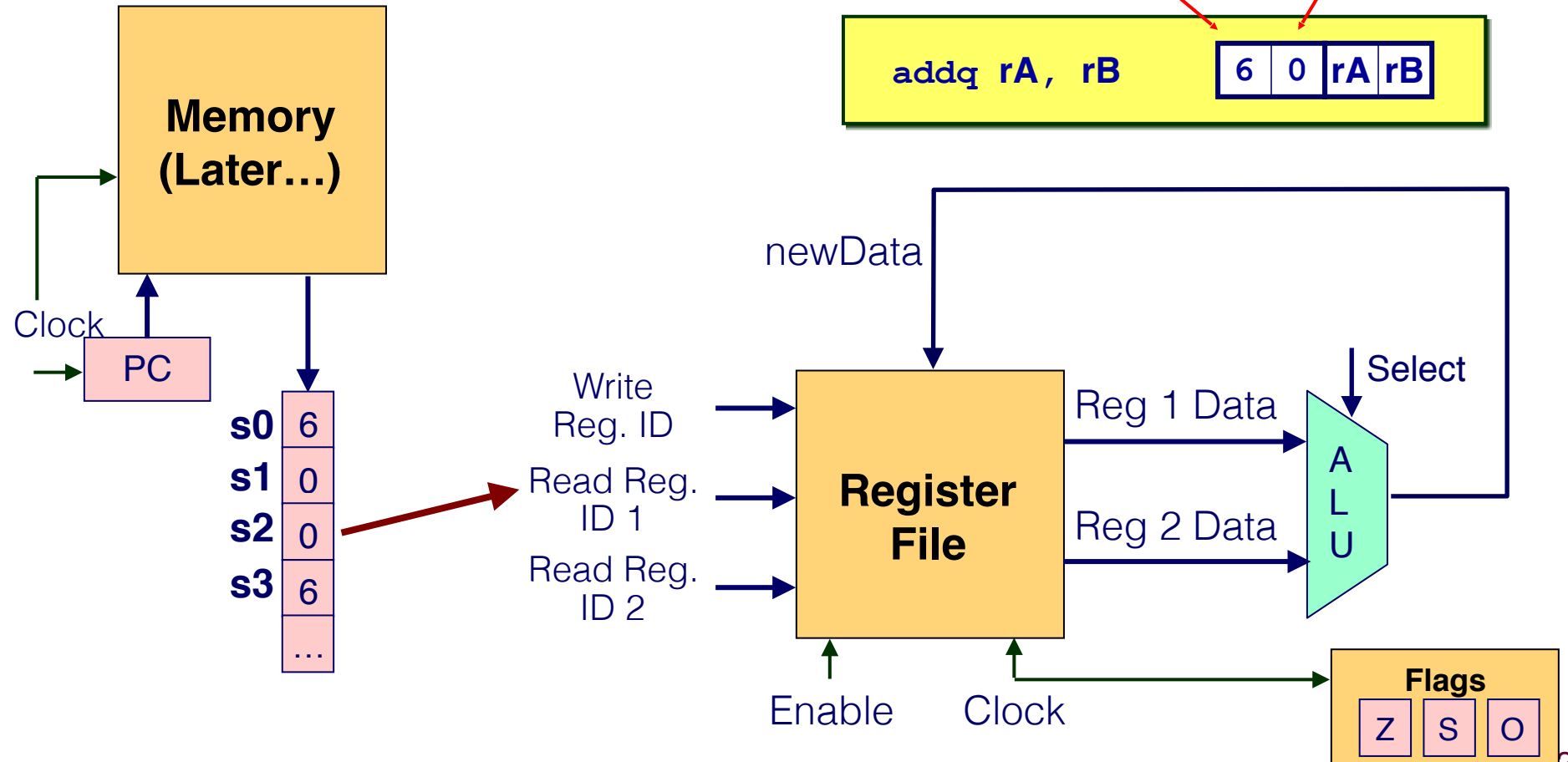

Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`


Instruction Code
Add

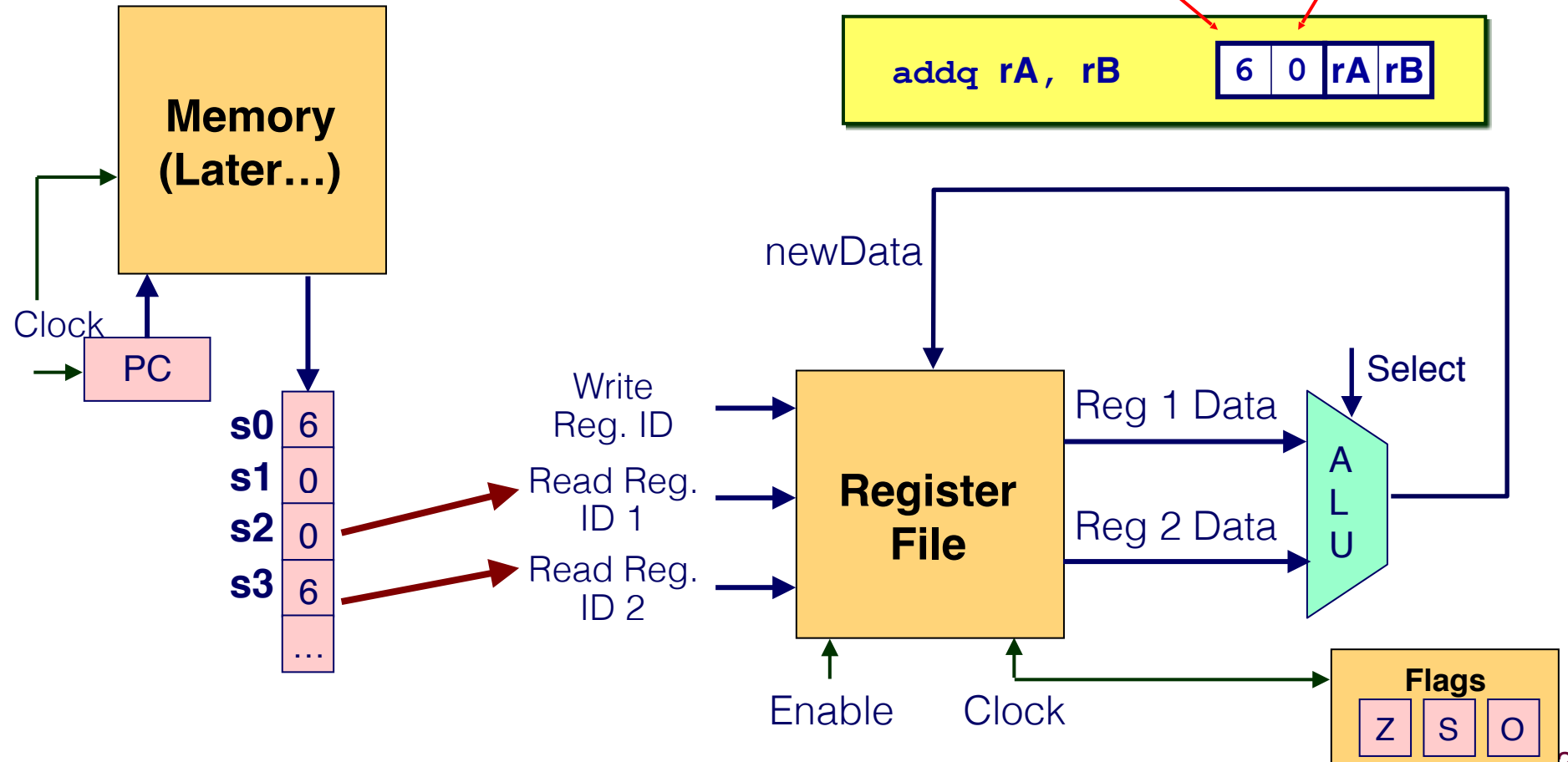

Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`


Instruction Code
Add

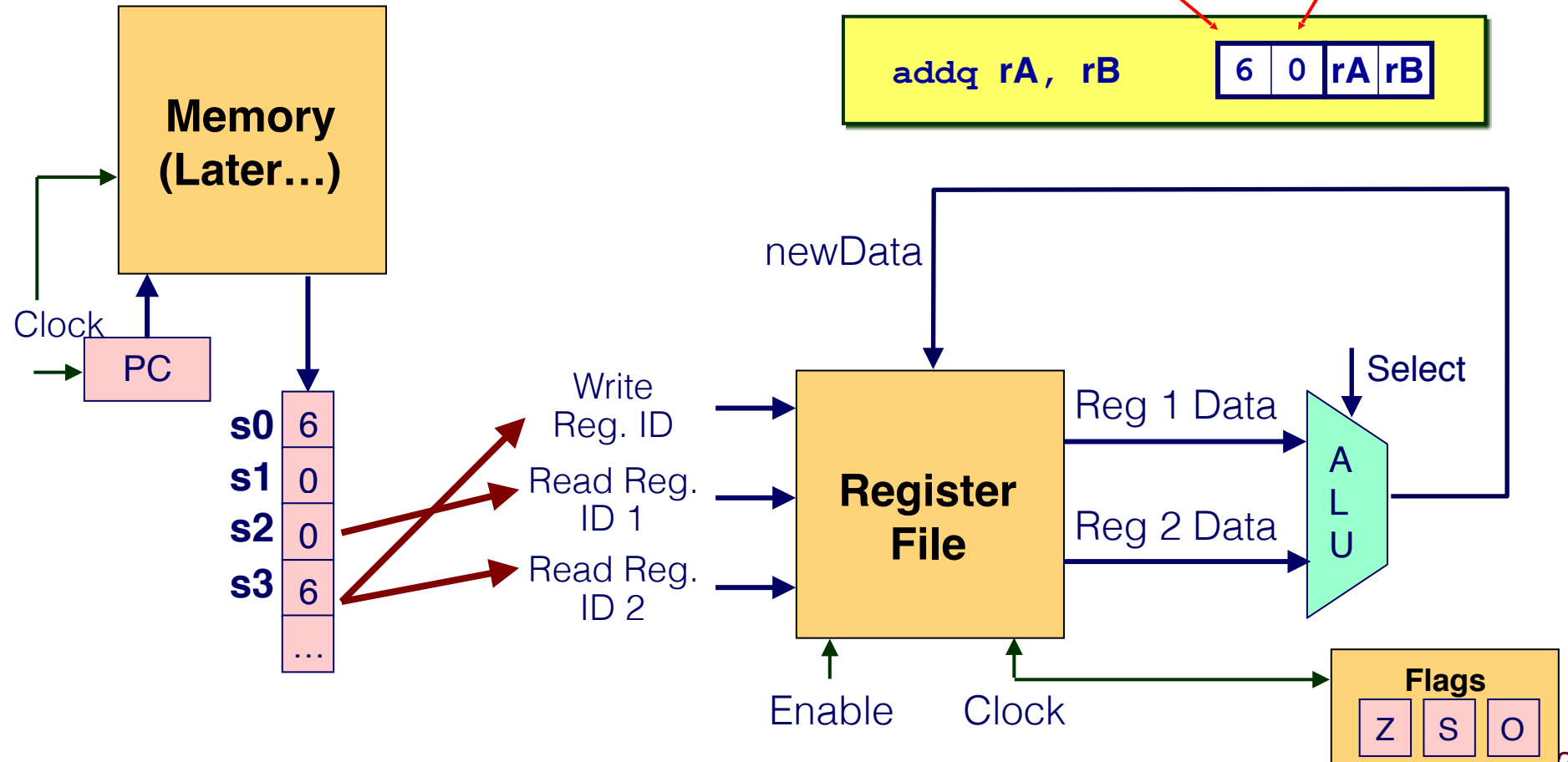

Executing an ADD instruction

- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`


Instruction Code
Add

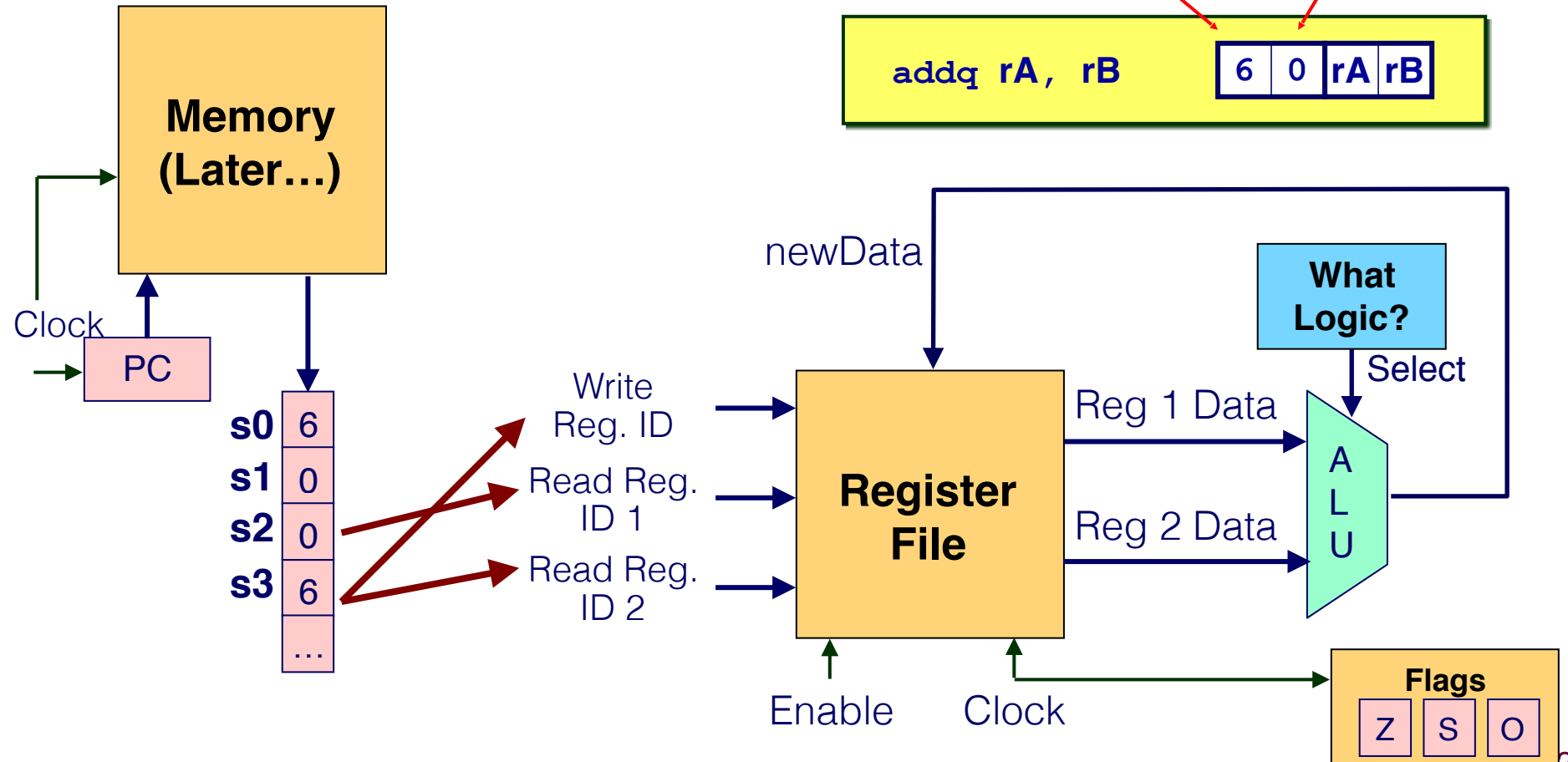

Executing an ADD instruction


- How does the processor execute `addq %rax, %rsi`
- The binary encoding is `60 06`

Instruction Code
Add

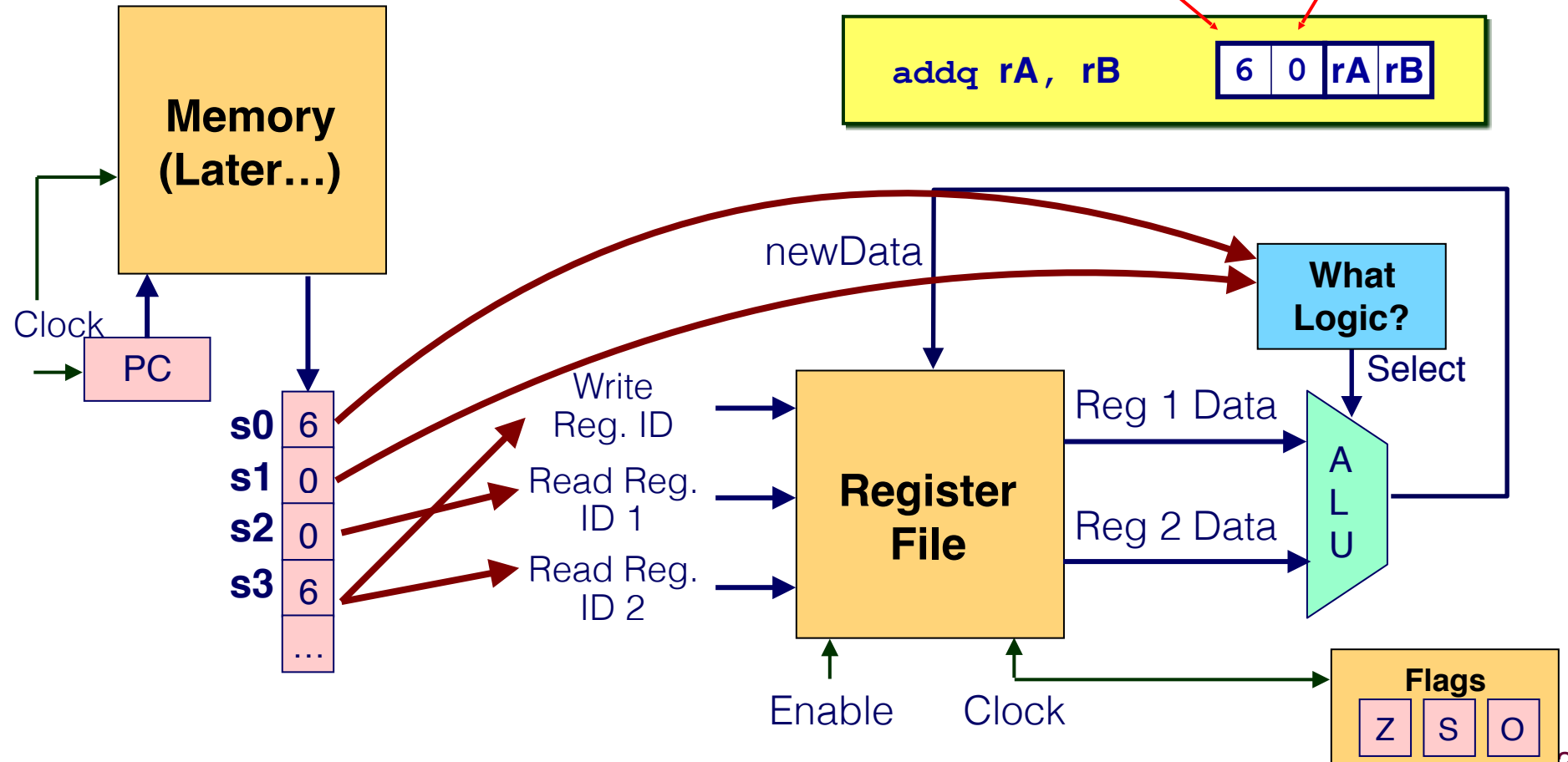


Executing an ADD instruction

- Logic 1: if (s0 == 6) select = s1;

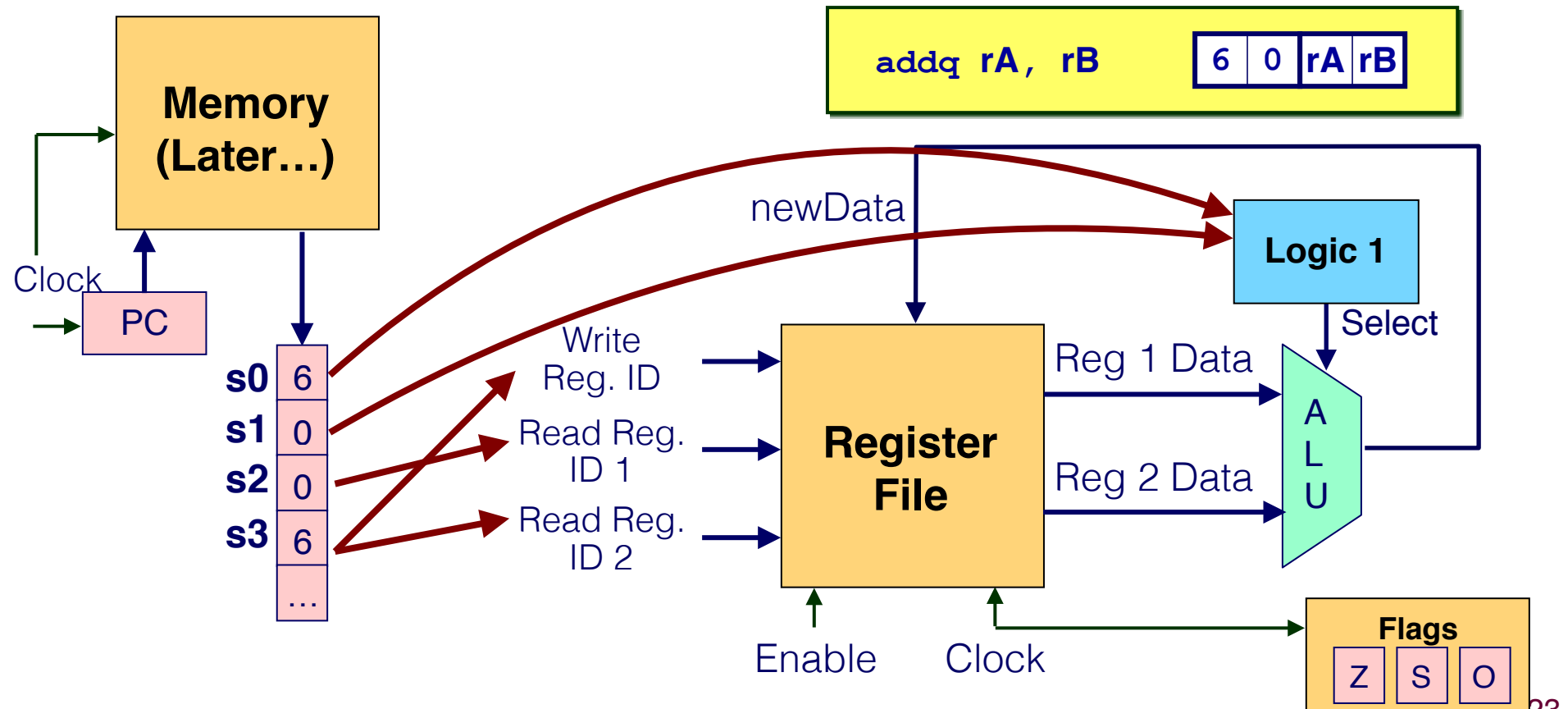


Executing an ADD instruction

- Logic 1: if (s0 == 6) select = s1;

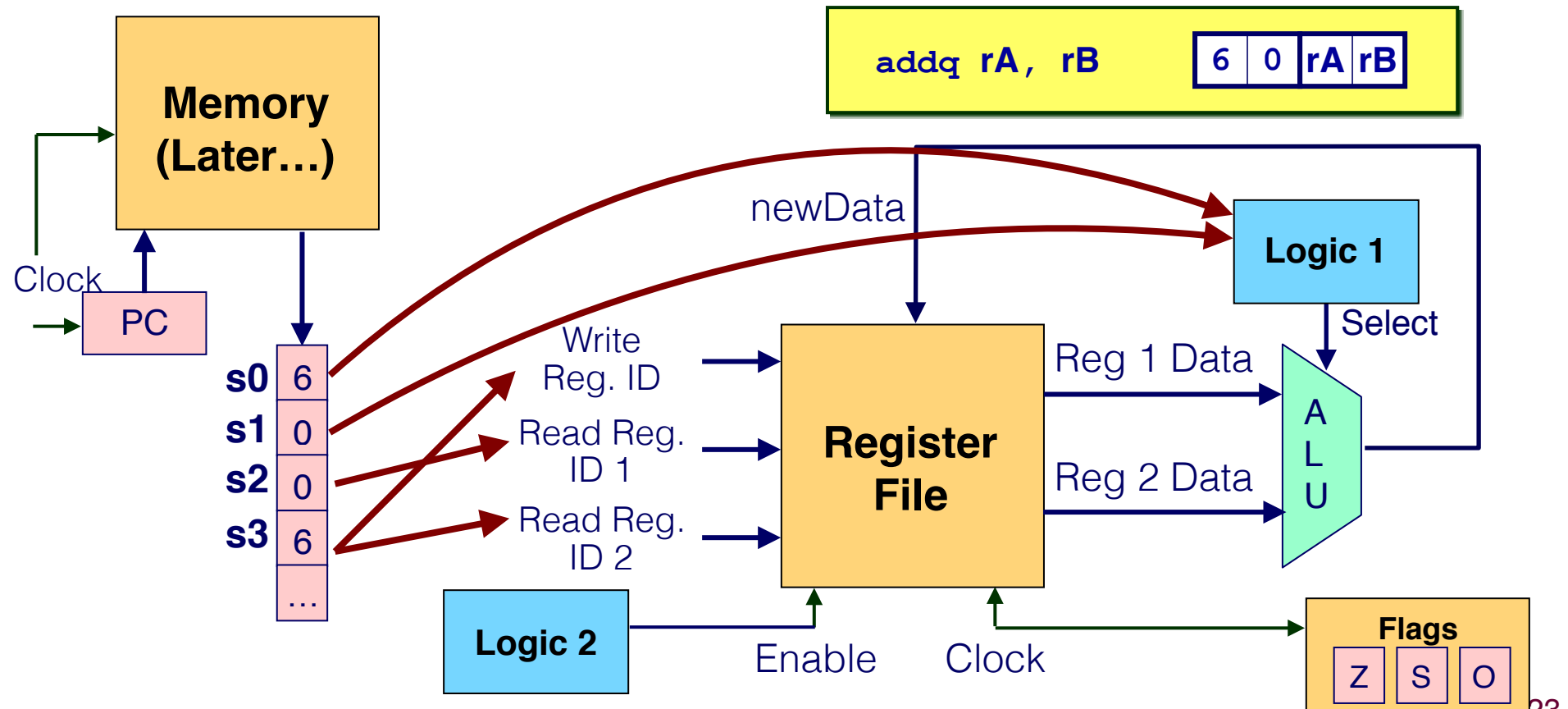


Executing an ADD instruction

- Logic 1: if (s0 == 6) select = s1;

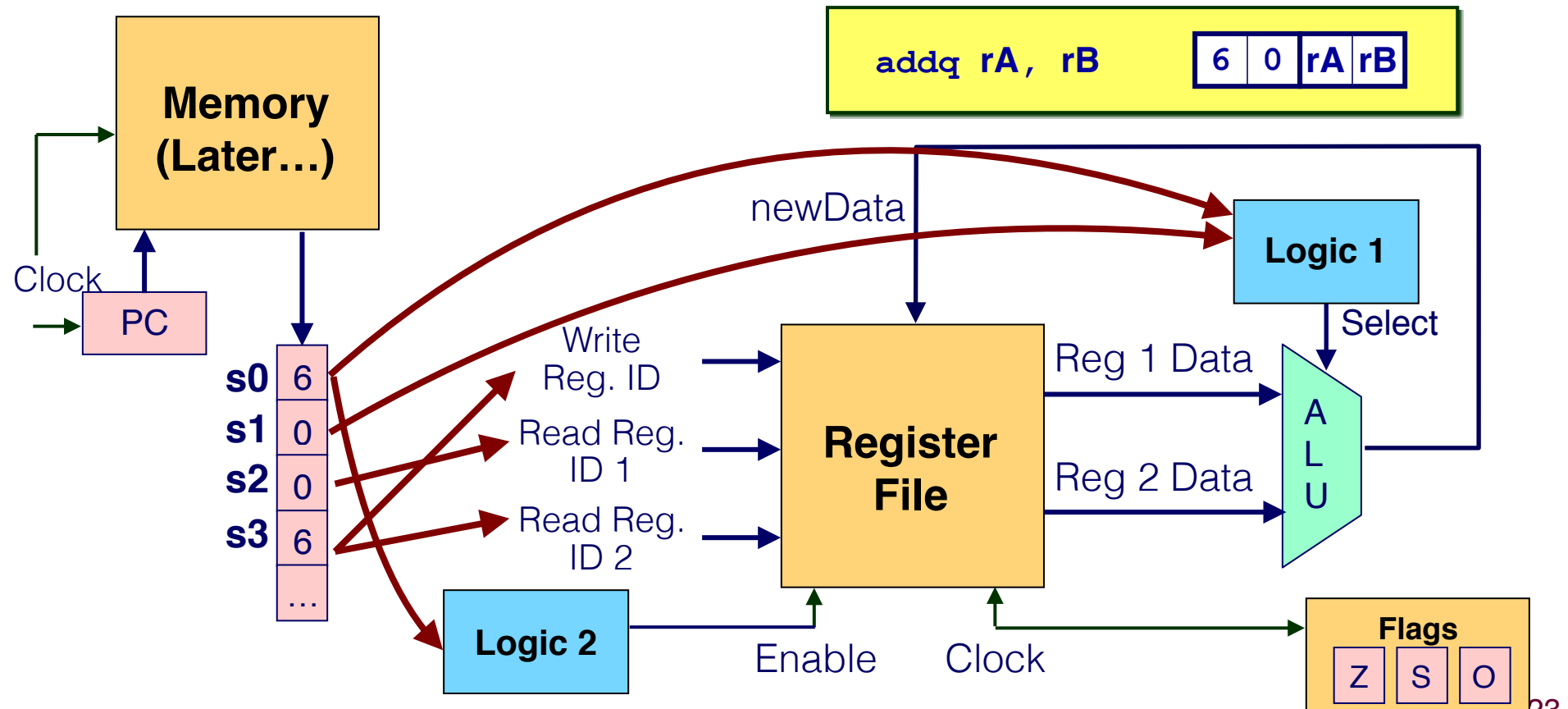


Executing an ADD instruction

 - Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;




Executing an ADD instruction

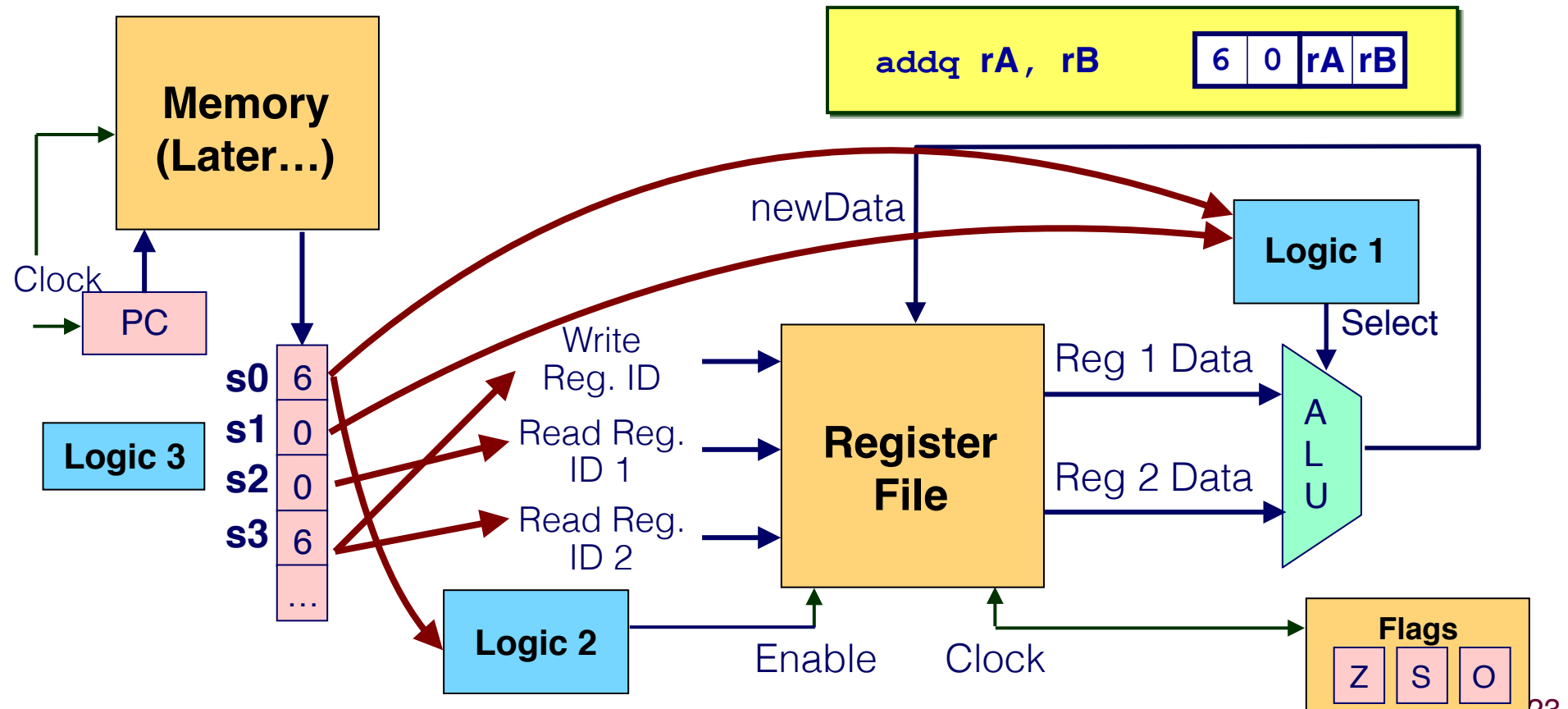- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;




Executing an ADD instruction

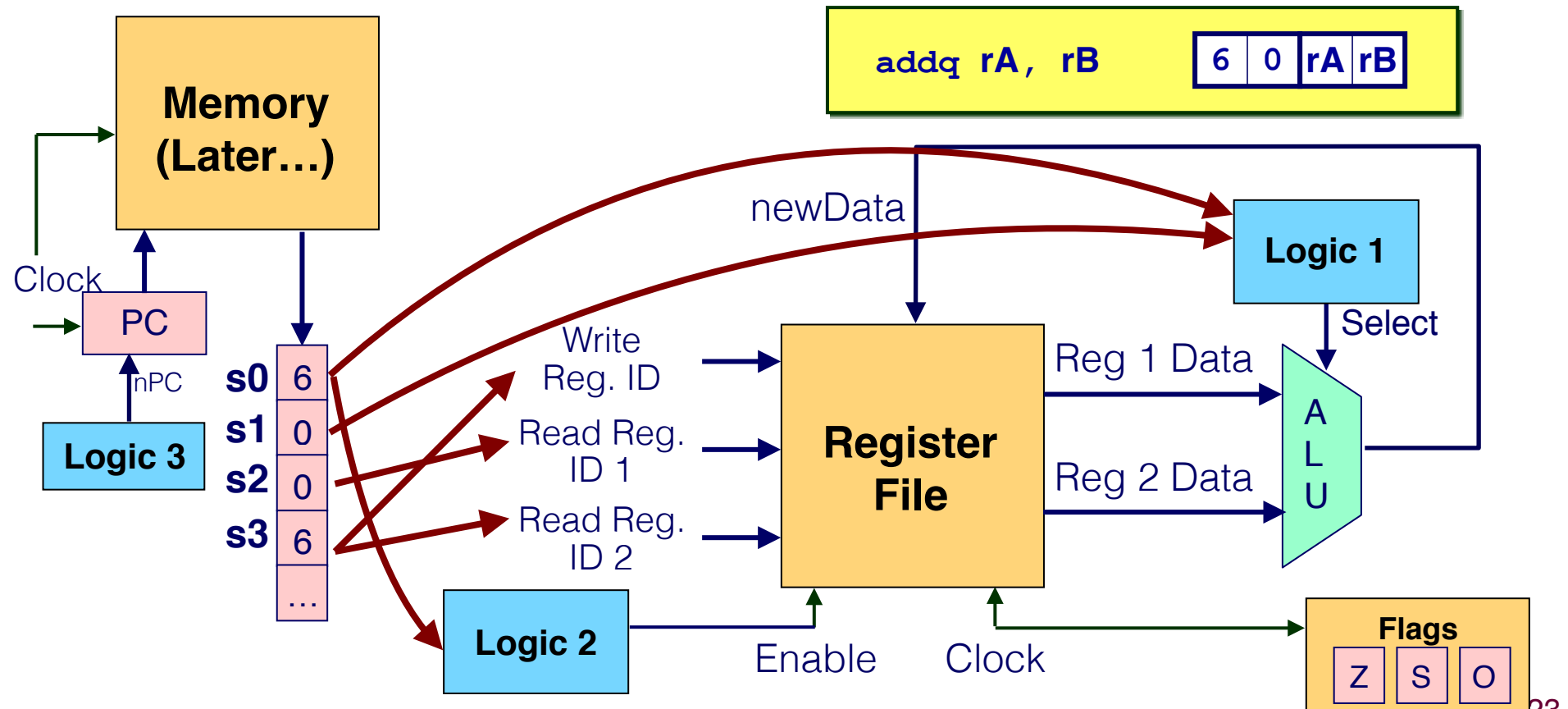- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;




Executing an ADD instruction

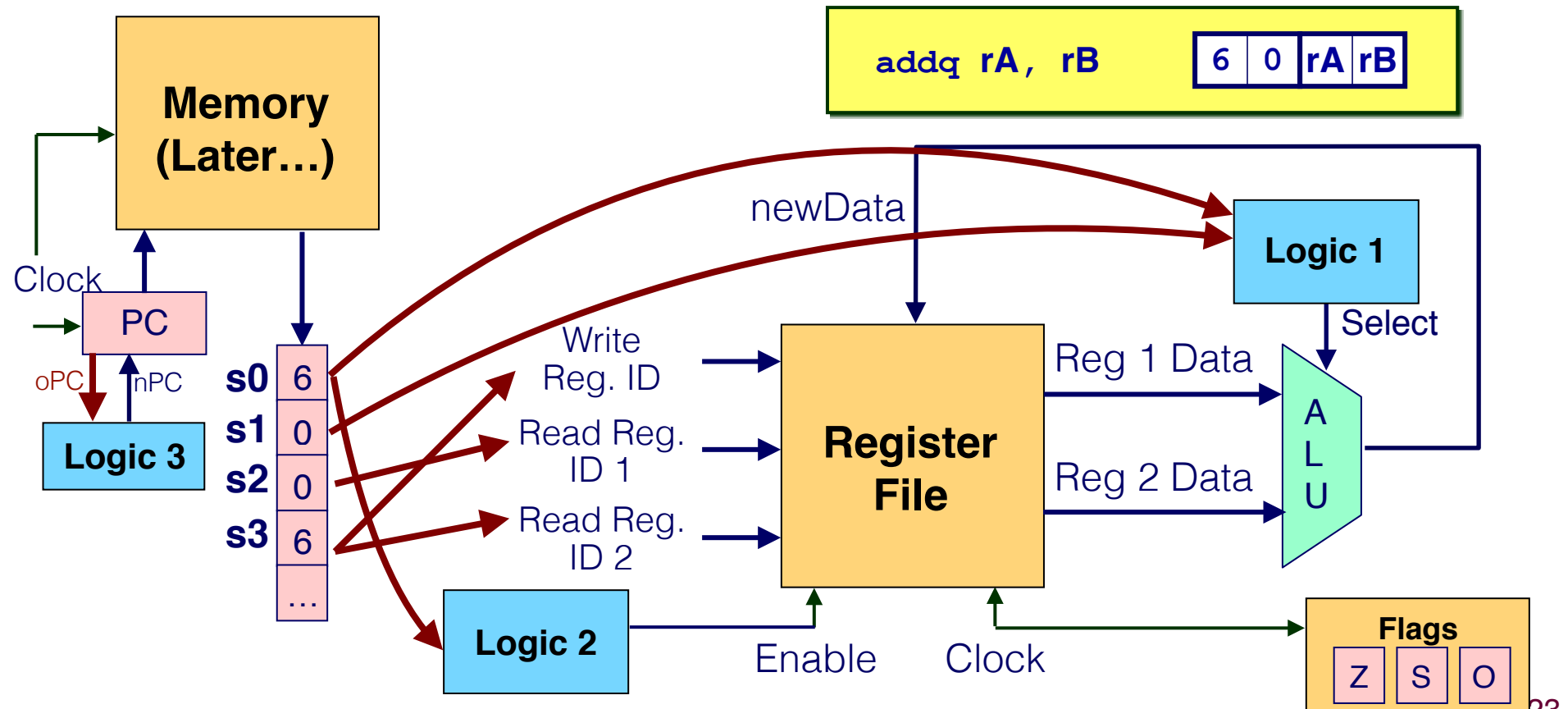- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;




Executing an ADD instruction

 - Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;




Executing an ADD instruction

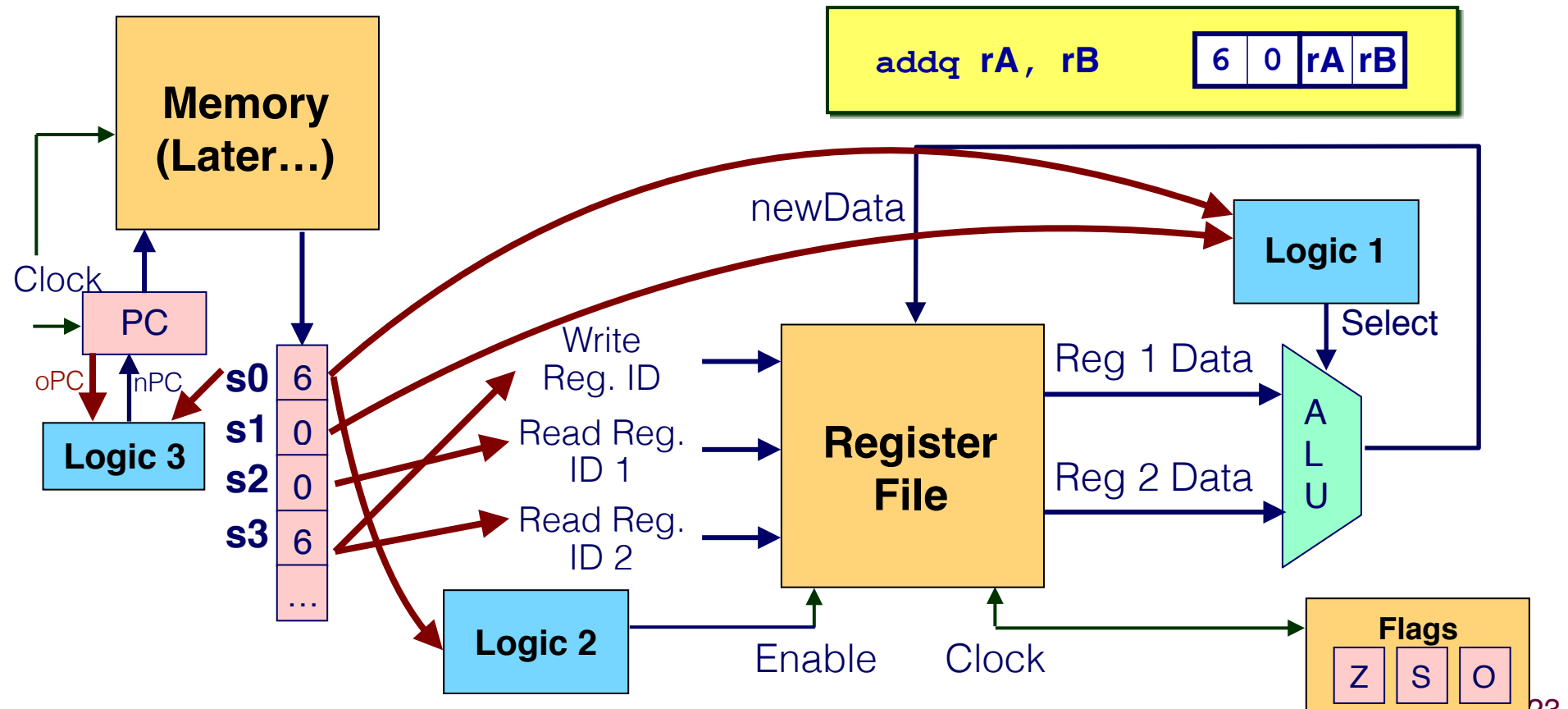- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;
- Logic 3: if (s0 == 6) nPC = oPC + 2;




Executing an ADD instruction

 - Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;
- Logic 3: if (s0 == 6) nPC = oPC + 2;
- How about Logic 4?



Executing an ADD instruction

 
- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;
- Logic 3: if (s0 == 6) nPC = oPC + 2;
- How about Logic 4?



Executing an ADD instruction

- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;
- Logic 3: if (s0 == 6) nPC = oPC + 2;
- How about Logic 4?


How do these logics get implemented?

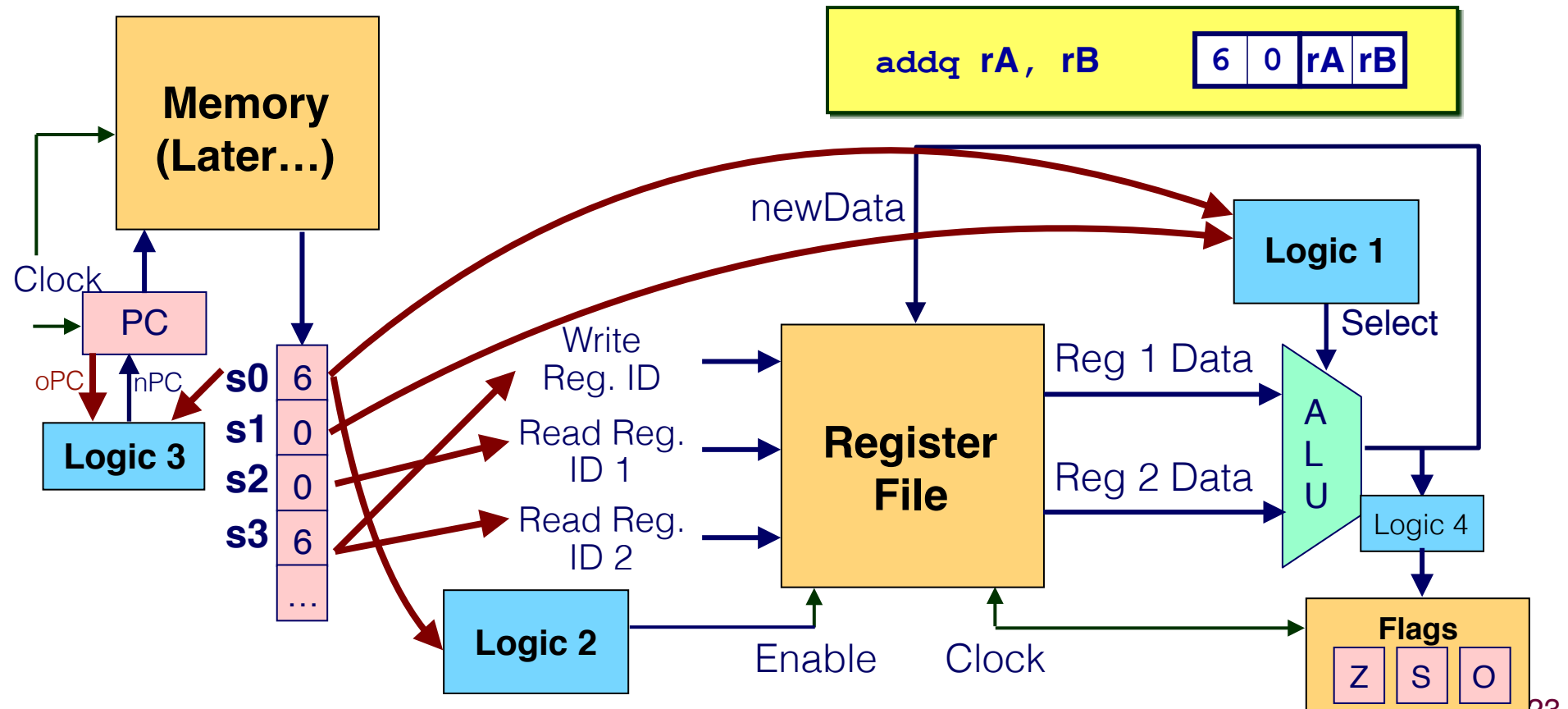

Executing an ADD instruction

- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;
- Logic 3: if (s0 == 6) nPC = oPC + 2;
- How about Logic 4?

How do these logics get implemented?

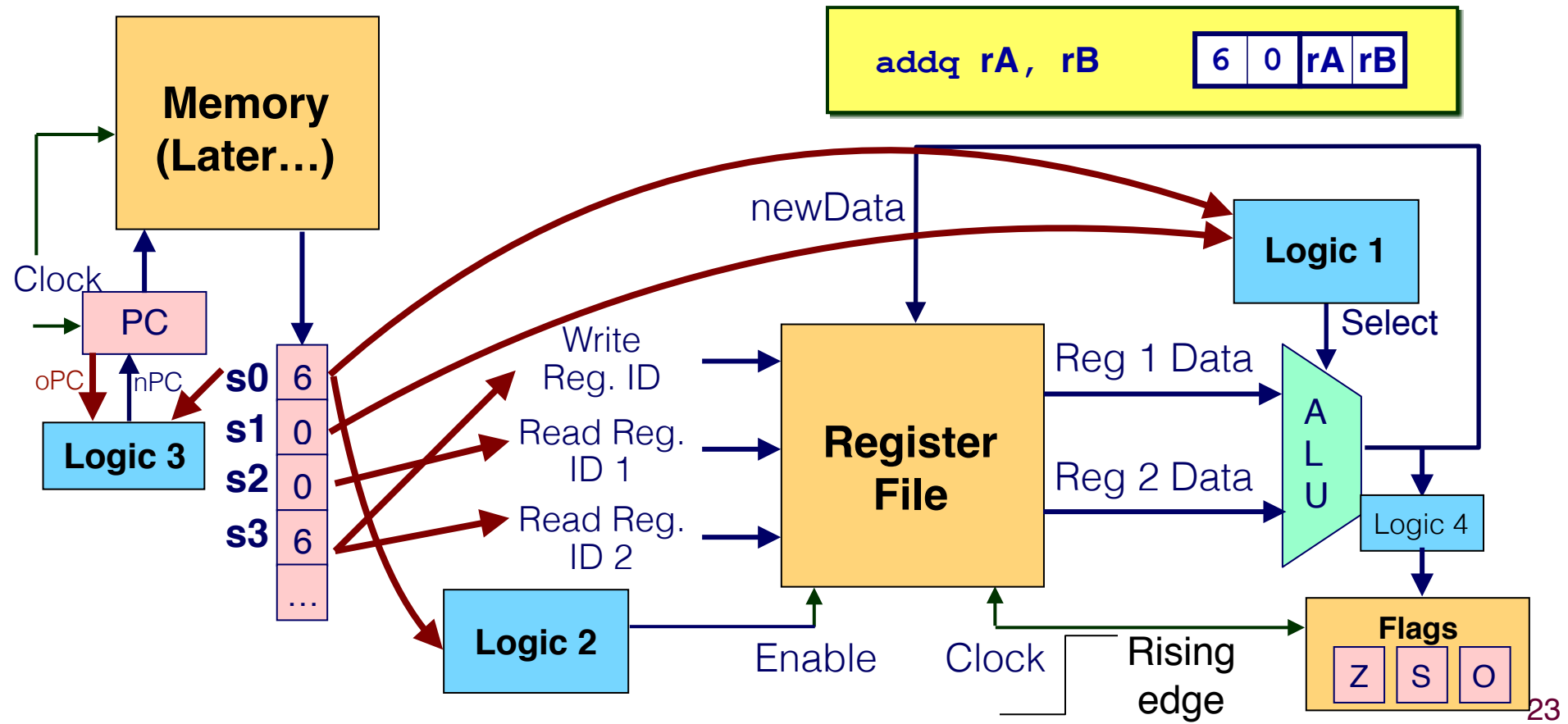

Executing an ADD instruction

- When the rising edge of the clock arrives, the RF/PC/Flags will be written.
- So the following has to be ready: newData, nPC, which means Logic1, Logic2, Logic3, and Logic4 has to finish.

